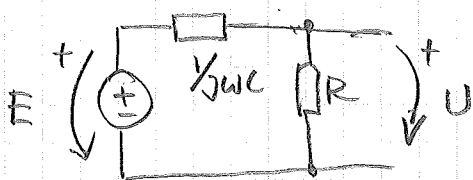


9.12



$$\left\{ \begin{array}{l} E = 10,0 e^{j\omega t} \text{ V} \\ \omega = 800 \text{ rad/s} \\ R = 1,25 \text{ k}\Omega \\ C = 500 \text{ nF} \end{array} \right.$$


Beräkna: $u(t) = |U| \sin(\omega t + \alpha)$

$$\begin{aligned} U &= \frac{R}{R + \frac{1}{j\omega C}} \cdot E \\ &= \frac{1,25 \cdot 10^3}{(1,25 \cdot 10^3 - j2500)} \cdot 10,0 e^{j\omega t} \\ &= \frac{1,25 \cdot 10,0}{(1,25 - j2,5)} e^{j\omega t} = \frac{12,5}{2,795 e^{-j63,4^\circ}} e^{j\omega t} \\ &= 4,47 e^{j(\omega t + 63,4^\circ)} \text{ A} \end{aligned}$$

$u(t) = \text{Im}\{U\} = 4,47 \sin(\omega t + 63,4^\circ) \text{ A}$

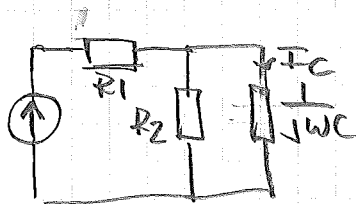9.13

$$\left\{ \begin{array}{l} I_e = 11,5 \text{ mA} \\ \beta = 0 \\ f = 50 \text{ Hz} \end{array} \right.$$




$$\left\{ \begin{array}{l} R_1 = 3,3 \text{ k}\Omega; R_2 = 2,3 \text{ k}\Omega \\ C = 1,0 \mu\text{F} \end{array} \right.$$

Bestäm $i_c(t) = |I_c| \sin(\omega t + \alpha)$

$$\begin{aligned} I_c &= \frac{R_2}{R_2 + \frac{1}{j\omega C}} \cdot I \\ &= \frac{2,3 \cdot 10^3}{2,3 \cdot 10^3 - j \frac{1}{2\pi \cdot 50 \cdot 1 \cdot 10^{-6}}} \cdot I_e \sqrt{2} e^{j\omega t} \\ &= \frac{2,3 \cdot 10^3}{2,3 \cdot 10^3 - j3,18 \cdot 10^3} \cdot 16,26 e^{j\omega t} \text{ mA} \\ &= \frac{2,3}{2,3 - j3,18} \cdot 16,26 e^{j\omega t} = \frac{2,3 \cdot 16,26}{3,98 e^{-j54,1^\circ}} e^{j\omega t} \\ &= 9,54 e^{j(\omega t + 54,1^\circ)} \text{ mA} \end{aligned}$$

$i_c(t) = \text{Im}\{I_c\} = 9,54 \sin(\omega t + 54,1^\circ) \text{ mA}$

9.14

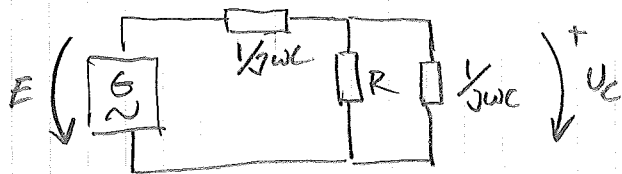

$$E = 600 e^{j(\omega t + 36^\circ)} \text{ mV} ; \omega = 5000 \text{ rad/s}$$

$$R = 10 \Omega ; C = 20 \mu\text{F}$$

Berapakah $U_C(t)$

$$U_C = \frac{R // \frac{1}{j\omega C}}{R // \frac{1}{j\omega C} + \frac{1}{j\omega C}} \cdot E$$

$$\left\{ \begin{array}{l} \times R // \frac{1}{j\omega C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC} \\ \times \frac{\frac{R}{(1 + j\omega RC)}}{\frac{R}{(1 + j\omega RC)} + \frac{1}{j\omega C}} = \frac{R}{R + \frac{(1 + j\omega RC)}{j\omega C}} \\ = \frac{R}{R + \frac{1}{j\omega C} + R} = \frac{R}{2R - j\frac{1}{\omega C}} \end{array} \right.$$

$$U_C = \frac{R}{2R - j\frac{1}{\omega C}} \cdot E = \frac{10}{(20 - j\frac{1}{5 \cdot 10^3 \cdot 20 \cdot 10^{-6}})} \cdot 600 e^{j36^\circ} e^{j\omega t}$$


$$= \frac{10}{(20 - j10)} 600 e^{j36^\circ} e^{j\omega t}$$

$$\frac{1}{(2 - j)}$$

$$= \frac{600 \cdot e^{j36^\circ}}{2,24 e^{j26,6^\circ}} e^{j\omega t} = 267,9 e^{j(\omega t + 62,6^\circ)} \text{ mV}$$

$$U_C(t) = \text{Im}\{U_C\} = 267,9 \sin(\omega t + 62,6^\circ) \text{ mV}$$

9.15

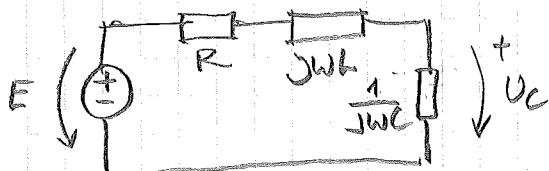

$R = 10 \Omega$
 $L = 10 \text{ mH} ; C = 5,0 \mu\text{F}$

$E = 600 e^{j(\omega t + 36,0^\circ)} \text{ mV} ; \omega = 5000 \text{ rad/s}$

Bestäm $U_C(t)$

$$U_C = \frac{\frac{1}{j\omega C} \cdot E}{\frac{1}{j\omega C} + R + j\omega L} = \frac{1}{1 + j\omega RC - \omega^2 LC} \cdot E$$

$$= \frac{1}{(1 - \omega^2 LC) + j\omega RC} \cdot E = \frac{1}{-0,25 + j0,25} \cdot E$$

$$1 - 25 \cdot 10^6 \cdot 10 \cdot 10^{-3} \cdot 5 \cdot 10^{-6}$$

$$= 1 - 1,25 = -0,25$$

$$5 \cdot 10^3 \cdot 10 \cdot 5 \cdot 10^{-6}$$


$$250 \cdot 10^{-3}$$

$$= \frac{0,6 \cdot e^{j36,0^\circ}}{0,354 e^{j135^\circ}}$$

$$e^{j\omega t} = 1,7 e^{j(\omega t - 99,0^\circ)} \quad \checkmark$$

$U_C(t) = \text{Im}\{U_C\} = 1,7 \sin(\omega t - 99,0^\circ) \text{ V}$

9.16

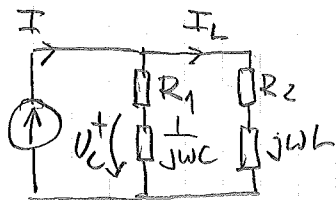

$$R_1 = 30 \Omega ; R_2 = 10 \Omega$$

$$C = 6,25 \mu\text{F} ; L = 17,5 \text{ mH}$$

$$I = 0,8 e^{j\omega t} ; \omega = 4000 \text{ rad/s}$$

a) Beräkna strömmen $i_L(t)$

$$\begin{aligned} I_L &= \frac{(R_1 + \frac{1}{j\omega C})}{(R_1 + \frac{1}{j\omega C}) + (R_2 + j\omega L)} \cdot I \\ &= \frac{(30 - j40)}{(30 + 10) + j(70 - 40)} \cdot I = \frac{30 - j40}{40 + j(70 - 40)} \cdot I \\ &= \frac{(3 - j4)}{(4 + j3)} \cdot 0,8 e^{j\omega t} = \frac{5 \cdot e^{-j53,1^\circ}}{5 \cdot e^{j36,9^\circ}} \cdot 0,8 e^{j\omega t} \\ &= 0,8 e^{j(\omega t - 90^\circ)} \text{ A} \end{aligned}$$


$$i_L(t) = \text{Im}\{I_L\} = 0,8 \sin(\omega t - 90^\circ) \text{ A}$$

b) Beräkna spänningen $u_C(t)$

$$\begin{aligned} U_C &= (I - I_L) \cdot \frac{1}{j\omega C} \\ &= (0,8 e^{j\omega t} - 0,8 e^{j(\omega t - 90^\circ)}) \cdot \frac{1}{j\omega C} \\ &= (0,8 - 0,8 e^{-j90^\circ}) e^{j\omega t} \cdot \frac{1}{j\omega C} \\ &= (0,8 + j0,8) \cdot \frac{1}{j\omega C} e^{j\omega t} \\ &= \frac{(0,8 + j0,8) e^{j\omega t}}{j 25 \cdot 10^{-3}} = \frac{1,13 \cdot e^{j45^\circ}}{0,025 \cdot e^{j90^\circ}} \cdot e^{j\omega t} \\ &= 45,2 e^{j(\omega t - 45^\circ)} \text{ V} \end{aligned}$$

$$u_C(t) = 45,2 \sin(\omega t - 45^\circ) \text{ V}$$

9.17

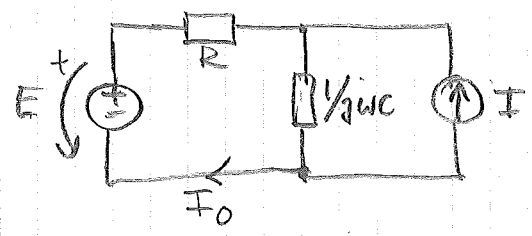

$R = 10 \Omega$
 $C = 10 \mu F$

$E = 25 e^{j\omega t} \text{ V} ; I = 2,5 e^{j\omega t} \text{ A} ; \omega = 10 \text{ krad/s.}$


a) Bestäm $i_0(t)$

$$\begin{aligned}
 I_0 &= \frac{E}{R + \frac{1}{j\omega C}} - \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot I \\
 &= \frac{E}{(10 - j10)} - \frac{-j10}{(10 - j10)} \cdot I \\
 &= \left(\frac{2,5}{\sqrt{2} e^{-j45^\circ}} - \frac{e^{-j90^\circ}}{\sqrt{2} e^{-j45^\circ}} \cdot 2,5 \right) e^{j\omega t} \\
 &= \left(\frac{2,5}{\sqrt{2}} e^{j45^\circ} - \frac{2,5}{\sqrt{2}} e^{-j45^\circ} \right) e^{j\omega t} \\
 &= \underbrace{(1,25 + j1,25) - (1,25 - j1,25)}_{j2,5} e^{j\omega t} \\
 &= 2,5 e^{j90^\circ} \cdot e^{j\omega t} = 2,5 e^{j(\omega t + 90^\circ)} \text{ A}
 \end{aligned}$$

$i_0(t) = \text{Im}\{I_0\} = 2,5 \sin(\omega t + 90^\circ) \text{ A}$

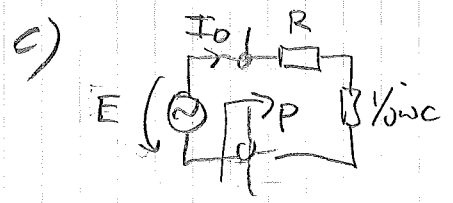b) Effektförbrukningen i R.

$P = R \cdot I_{0e}^2 = 10 \cdot \left(\frac{2,5}{\sqrt{2}}\right)^2 = \underline{\underline{31,25 \text{ W}}}$




$P_E = E \cdot I_0 \cdot \cos(\varphi) ; \varphi = -90^\circ$
 $E = 25 e^{j\omega t}$
 $I_0 = 2,5 e^{j(\omega t + 90^\circ)} \Rightarrow \underline{\underline{P_E = 0}}$

All aktiv effekt måste komma från I

$\underline{\underline{P_I = R \cdot (I_{0e})^2}}$
 $= 10 \cdot \left(\frac{2,5}{\sqrt{2}}\right)^2 = \underline{\underline{31,25 \text{ W}}}$

9.18

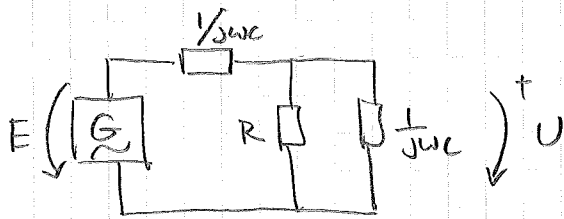

$$U = \frac{R // \frac{1}{j\omega C}}{R // \frac{1}{j\omega C} + \frac{1}{j\omega C}} \cdot E$$

dar $R // \frac{1}{j\omega C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$

$$\Rightarrow U = \frac{\frac{R}{1 + j\omega RC}}{\frac{R}{1 + j\omega RC} + \frac{1}{j\omega C}} \cdot E = \frac{\frac{j\omega RC}{1 + j\omega RC}}{\frac{j\omega RC}{1 + j\omega RC} + 1} \cdot E$$

$$= \frac{j\omega RC}{j\omega RC + 1(1 + j\omega RC)} \cdot E = \frac{j\omega RC}{1 + j2\omega RC} \cdot E$$

$$F(\omega) = \frac{U}{E} = \frac{j\omega RC}{1 + j2\omega RC} = \frac{|U|}{|E|} e^{j(90^\circ - \arctan(2\omega RC))} = \frac{|F(\omega)|}{|E|} e^{j \text{Arg} F(\omega)}$$

a) Vid vilken frekvens ligger u 45° fr̄e generatorspanningen e?

$$\Rightarrow \text{Arg}\{F(\omega)\} = 45^\circ \Rightarrow 90^\circ - \arctan(2\omega RC) = 45^\circ$$

$$\arctan(2\omega RC) = 45^\circ$$

$$2\omega RC = 1 \Rightarrow \omega = \frac{1}{2RC}$$

b) Vid vilken frekvens är $U_e = 0,25 \cdot E_e$

$$|F(\omega)| = \frac{|U|}{|E|} = \frac{U_e}{E_e} = 0,25$$

$$\Rightarrow \frac{|j\omega RC|}{|1 + j2\omega RC|} = \frac{1}{4}$$

$$\frac{\omega RC}{\sqrt{1^2 + (2\omega RC)^2}} = \frac{1}{4}$$

$$\frac{(\omega RC)^2}{1^2 + (2\omega RC)^2} = \frac{1}{16}$$

$$16(\omega RC)^2 = 1 + 4(\omega RC)^2$$


$$12\omega^2(RC)^2 = 1$$

$$\omega^2 = \frac{1}{12(RC)^2}$$

$$\omega = \frac{1}{2\sqrt{3}RC}$$


9.19

Komplext
Schema

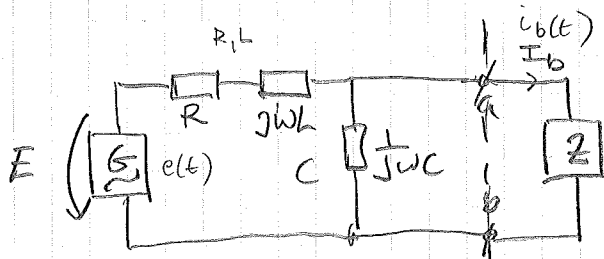

$E = 16 e^{j\omega t} \text{ V}$, $\omega = 100 \text{ krad/s}$
 $R = 4 \Omega$, $L = 30 \mu\text{H}$
 $C = 1,667 \mu\text{F}$

a) Äquivalent tråpol:

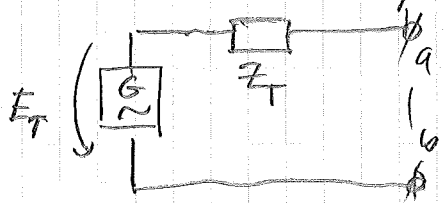

$$E_T = \frac{1/j\omega C}{\frac{1}{j\omega C} + (R + j\omega L)} \cdot E = \frac{1}{(1 - \omega^2 LC + j\omega RC)} \cdot E$$

$$= \frac{1}{(1 - 10^4 \cdot 30 \cdot 10^{-6} \cdot 1,667 \cdot 10^{-6}) + j10^5 \cdot 4 \cdot 1,667 \cdot 10^{-6}} \cdot E = \frac{1}{0,5 + j0,667} \cdot E$$

$$= \frac{1 \cdot e^{j0^\circ}}{0,834 \cdot e^{j53,1^\circ}} \cdot 16 \cdot e^{j\omega t} = \frac{16 \cdot 1}{0,834} e^{j(\omega t - 53,1^\circ)} = 19,2 e^{j(\omega t - 53,1^\circ)} \text{ V}$$


$$Z_T = (R + j\omega L) \parallel \frac{1}{j\omega C} = \frac{(R + j\omega L) \cdot \frac{1}{j\omega C}}{(R + j\omega L) + \frac{1}{j\omega C}}$$

$$= \frac{(4 + j10^5 \cdot 30 \cdot 10^{-6})}{(1 - 10^4 \cdot 30 \cdot 10^{-6} \cdot 1,667 \cdot 10^{-6}) + j10^5 \cdot 4 \cdot 1,667 \cdot 10^{-6}}$$

$$= \frac{4 + j3}{0,5 + j0,667} = \frac{5 \cdot e^{j36,9^\circ}}{0,834 \cdot e^{j53,1^\circ}} \approx 6,0 e^{-j16,2^\circ}$$

$$= (5,76 - j1,67) \Omega$$

b) Lasten $Z = R = 2 \Omega$.

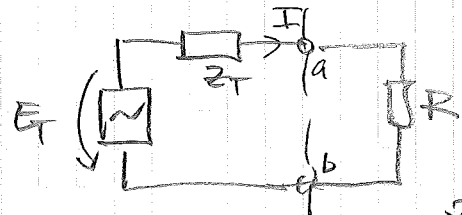

Suboptimalt om: $R = |Z_T| = 6,2 \rightarrow P = 7,8 \text{ W}$

Bestäm $i(t)$ om P i lasten
då $Z = R = 2 \Omega$.

$$I = \frac{E_T}{(Z_T + R)} = \frac{19,2 \cdot e^{j(\omega t - 53,1^\circ)}}{(5,76 - j1,67) + 2} = \frac{19,2 e^{-j53,1^\circ} e^{j\omega t}}{7,94 \cdot e^{j21,1^\circ}} \approx 2,42 e^{j(\omega t - 41^\circ)} \text{ A}$$

$$i(t) = \text{Im}\{I\} = 2,42 \sin(\omega t - 41^\circ) \text{ A}$$


$$P = R \cdot I_e^2 = 2 \cdot \left(\frac{2,42}{\sqrt{2}}\right)^2 = (2,42)^2 = 5,86 \text{ W}$$

9.19) foto
c)

Z_L kan väljas fritt.

Bestäm Z_L för maximal effektutv. P
Bestäm P .
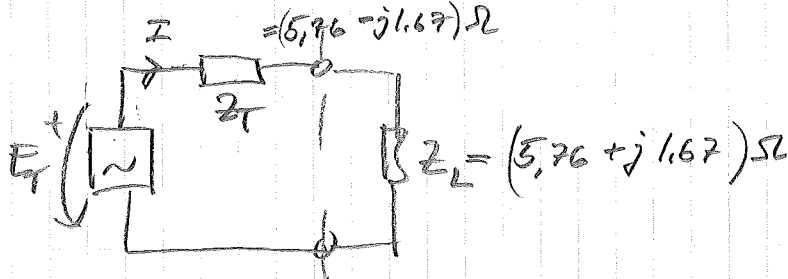
$$Z_L = \overline{Z_T} = \overline{(5,76 - j1,67)} = \underline{\underline{(5,76 + j1,67)\Omega}}$$



$$P = R_L \cdot I_e^2$$

$$\left\{ \begin{array}{l} R_L = 5,76 \Omega \\ I = \frac{E_T}{(Z_T + Z_L)} = \frac{E_T}{2 \cdot 5,76} = \frac{19,2 \cdot e^{j(\omega t - 53,7^\circ)}}{2 \cdot 5,76} \\ \quad = 1,67 e^{j(\omega t - 53,7^\circ)} \text{ A} \end{array} \right.$$

Således $I_e = 1,67/\sqrt{2}$ A

$$\Rightarrow P = R_L \cdot I_e^2 = 5,76 \cdot \left(\frac{1,67}{\sqrt{2}}\right)^2 = \underline{\underline{8W}}$$