


# Svar till tenta Elektronik 9k 8/1-04

A1. Minsta  $R_1$  blir  $\frac{10V}{20\mu A} = R_1 + R_2 =$   
 $= R_1 + 400\Omega = 500\Omega \Rightarrow R_1 = 100\Omega$

$$A_V = \frac{R_1 + R_2}{R_1} = \frac{100 + 400}{100} = 5,99$$


A2.  $I_{DZ} = \frac{25V - 0,6V}{20k} = \frac{24,4V}{20k} = 1,22mA$
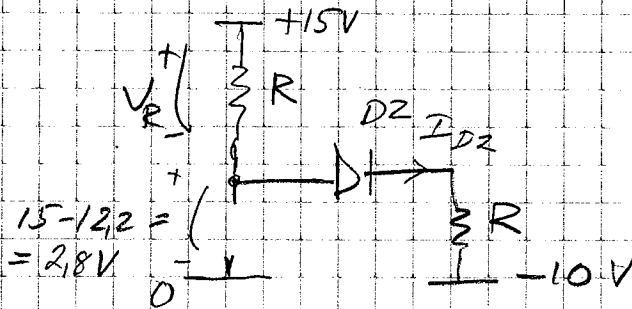
$$V_R = R \cdot I_{DZ} = 10 \cdot 1,22 = 12,2V$$




$I_{D1} = 0$  ty  
 dioden ligger back-  
 spänd.

A3.  $V_{IN} = +10V \Rightarrow$

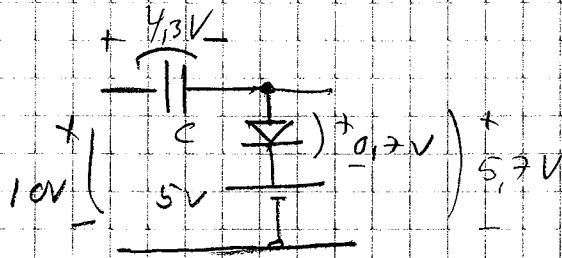

Kondensatorspän  $\approx 4,3V$  [hinne i te  
 laddas ur då  $V_{IN} < +10V$ ].


$$V_{OUT} = V_{IN} - 4,3V$$

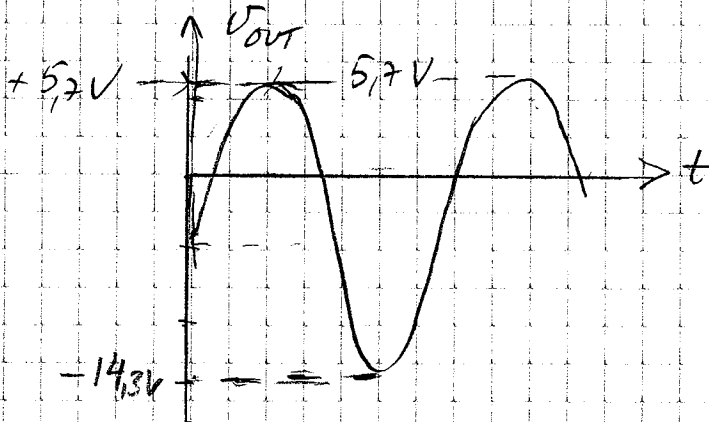



A4/ Koppla ett lastmotstånd på utgången.  
 Då utspänning sjunkit till hälften är  
 $P_{\text{last}} = P_{\text{out}}$ .  $\therefore P_{\text{out}}$  kan avläsas  
 på lastmotståndet.

A5/


$V_{in} > 0,7V + 0,7V$

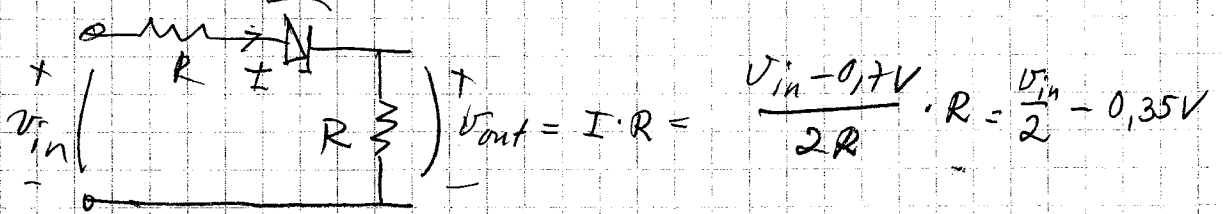

$V_{in} < -4,7V$

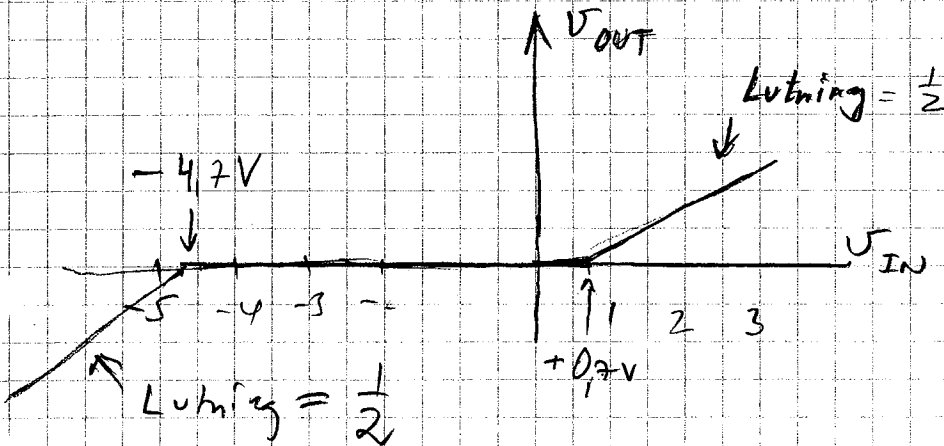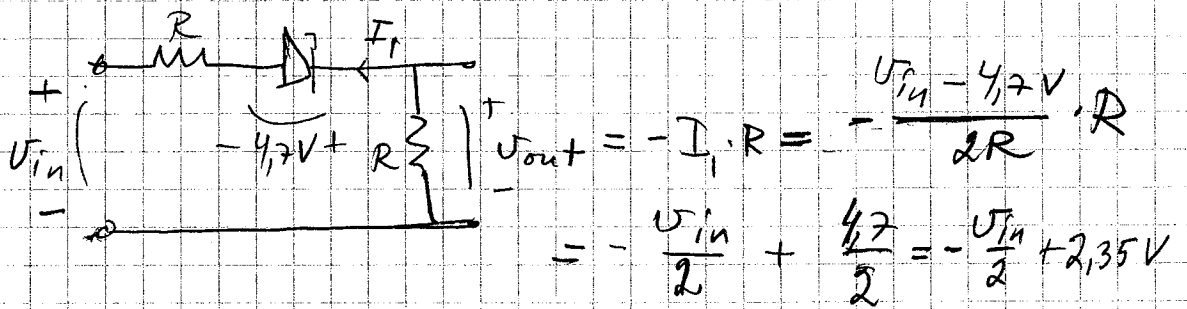

A6/

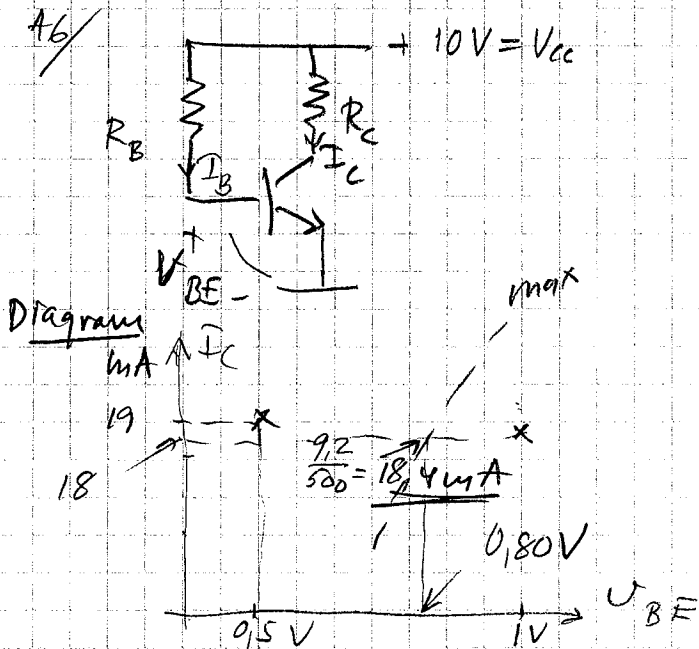

$$\begin{cases} V_{cc} = I_B \cdot R_B + V_{BE} \\ \text{där } I_B = \frac{I_C}{\beta} \end{cases}$$

$$V_{cc} = I_C \cdot \frac{R_B}{\beta} + V_{BE}$$

$$10V = I_C \cdot \frac{100k\Omega}{200} + V_{BE}$$


$$\Rightarrow 10 = I_C \cdot 500 + V_{BE}$$

$$V_{BE} = 1V \Rightarrow I_C = \frac{9}{500} = 18 \mu A$$


$$V_{BE} = 0,5V \Rightarrow I_C = \frac{9,5}{500} = 19 \mu A$$

Kurvan  $\Rightarrow V_{BEQ} = 0,80V \quad I_{CQ} = 18,4 \mu A$

A7/

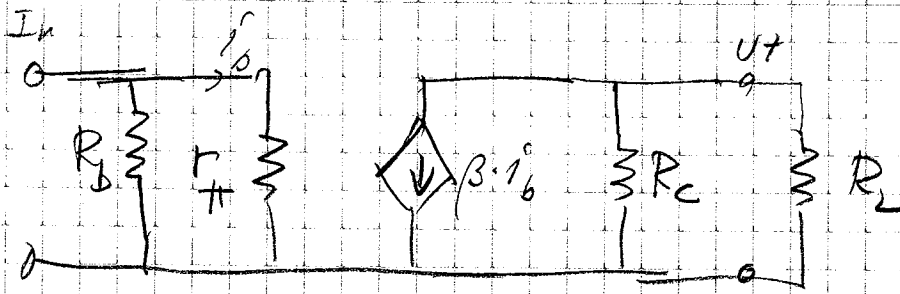


A8/

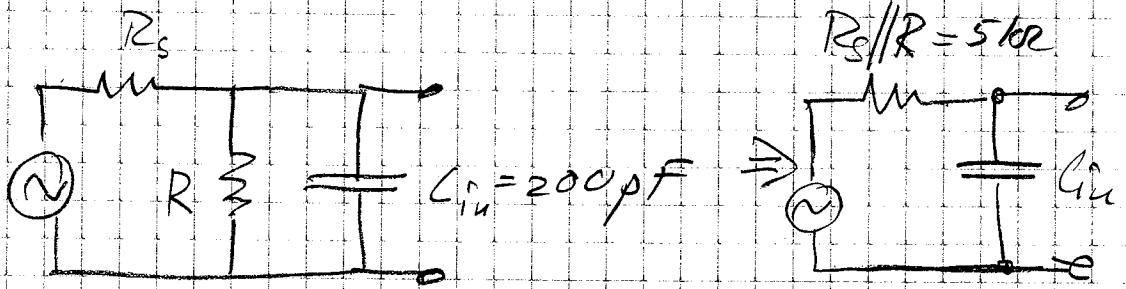

$$f_H = \frac{1}{2\pi C_{in} (R_s \parallel R)} = \frac{1}{2\pi \cdot 200 \cdot 10^{-12} \cdot 5 \cdot 10^3} = 159 \text{ kHz}$$

A9/

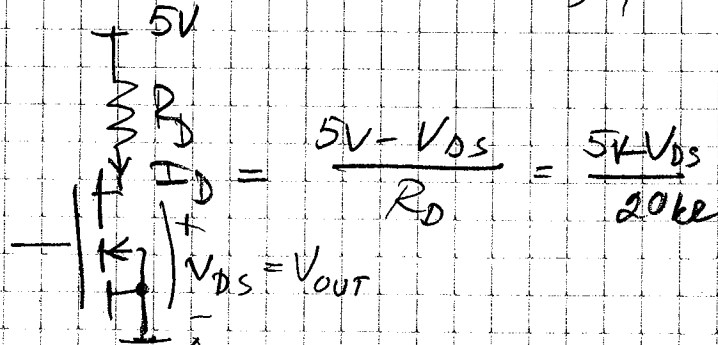Triod region:  $I_D = K(2(V_{GS} - V_{to})V_{DS} - V_{DS}^2)$   
 $= 50(2(5-2)V_{DS} - V_{DS}^2) \mu A$



$$\therefore I_D = \frac{5V - V_{DS}}{20k\Omega} = 50 \mu A/V^2 (6V_{DS} - V_{DS}^2)$$

$$\Rightarrow 5 - V_{DS} = 6V_{DS} - V_{DS}^2$$


$$\Rightarrow V_{DS}^2 - 7V_{DS} + 5 = 0 \Rightarrow V_{DS} = 3,5 \pm \sqrt{3,5^2 - 5}$$

$$= 3,5 \pm 2,69 = \underline{\underline{0,81 V}}$$

A10/

$X = \overline{A \cdot B}$  (NAND-gate)

B1/

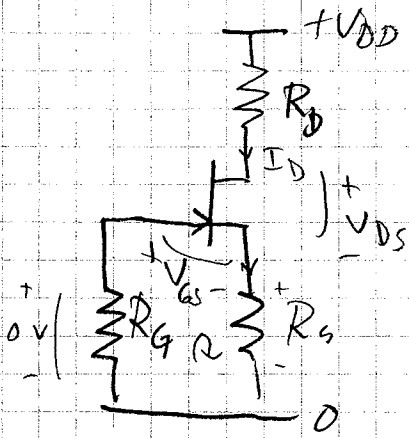

$$\textcircled{1} \quad V_{GS} + I_D \cdot R_S = 0 \quad (1)$$

$$\textcircled{2} \quad V_{DD} = I_D \cdot R_D + V_{DS} + I_D \cdot R_S \quad (2)$$

$$I_D = K \cdot (V_{GS} - V_{to})^2 \quad (3)$$

$$\text{d\u00e4r } K = \frac{I_{DSS}}{V_{to}^2} = \frac{12 \text{ mA}}{16 \text{ V}^2}$$

$$(3) \rightarrow (1) \Rightarrow V_{GS} + K(V_{GS} - V_{to})^2 \cdot R_S = 0$$

$$\Rightarrow V_{GS} + \frac{12 \text{ mA}}{(-4 \text{ V})^2} (V_{GS} + 4 \text{ V})^2 \cdot 0,28 \text{ k}\Omega = 0$$

$$\Rightarrow V_{GS} + 0,21 (V_{GS} + 4 \text{ V})^2 = 0$$

$$\Rightarrow 4,76 \cdot V_{GS} + V_{GS}^2 + 8 \cdot V_{GS} + 16 = 0$$

$$\Rightarrow V_{GS}^2 + 12,76 V_{GS} + 16 = 0 \Rightarrow V_{GS} = -6,38 \pm \sqrt{40,7 - 16}$$

$$V_{GS} = -1,4084 \text{ V}$$

$$(1) \Rightarrow -1,4 \text{ V} + I_D \cdot 0,28 \text{ k}\Omega = 0 \Rightarrow$$


$$\Rightarrow I_D = \frac{1,4}{0,28} = 5,03 \text{ mA} \approx \underline{\underline{5,0 \text{ mA}}} = I_{DQ}$$

$$(2) \Rightarrow V_{DS} = V_{DD} - I_D (R_D + R_S) = 18 \text{ V} - 5 \text{ mA} (2 + 0,28) \text{ k}\Omega$$

$$= 6,53 \approx \underline{\underline{6,5 \text{ V}}}$$

B2/

Elw. Signalschema

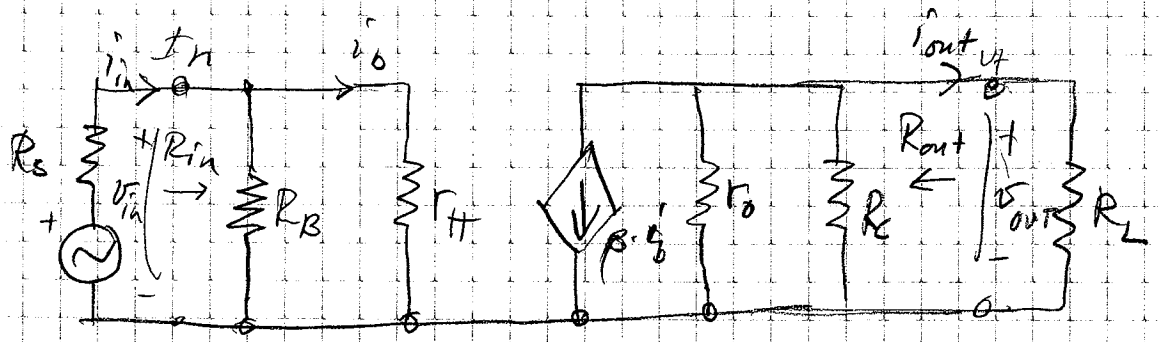

$$R_{in} = R_B \parallel r_{\pi} = 15 \text{ M}\Omega \parallel 2,6 \text{ k}\Omega \approx 2,595 \approx \underline{\underline{2,6 \text{ k}\Omega}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_{CQ}}{V_T}} = \frac{200 \cdot 0,026}{2 \text{ mA}} = 2,6 \text{ k}\Omega$$

$$R_{out} = r_o \parallel R_C = 50 \parallel 5 = 4,545 \approx \underline{\underline{4,5 \text{ k}\Omega}}$$


$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot (r_o \parallel R_C \parallel R_L)$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2}{0,026} = 76,92 \text{ mA/V}$$

$$A_v = \frac{v_{out}}{v_{in}} = -76,92 \text{ mA/V} \cdot \left( \frac{50 \text{ k}\Omega \parallel 5 \text{ k}\Omega \parallel 10 \text{ k}\Omega}{3,125 \text{ k}\Omega} \right) = -240,99$$

$$A_i = \frac{i_{out}}{i_{in}} = \frac{\frac{v_{out}}{R_L}}{\frac{v_{in}}{R_{in}}} = \frac{v_{out}}{v_{in}} \cdot \frac{R_{in}}{R_L} = -240 \cdot \frac{2,6}{10} = \underline{\underline{-62,599}}$$

B3/

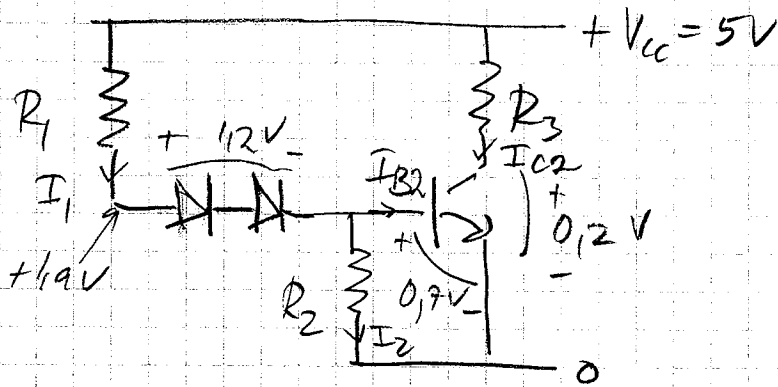

Sämsta fallet då  $\beta = 100$  (min-värde)

$$I_{C2} = \frac{5V - 0,2V}{R_3} = \frac{4,8}{50} = 96 \mu A$$

$$\Rightarrow I_{B2} = \frac{I_{C2}}{\beta_{min}} = \frac{96}{100} = 0,96 \mu A$$


$$I_2 = \frac{V_{BE}}{R_2} = \frac{0,7V}{500\Omega} = 1,4 \mu A$$

$$I_1 = \frac{5V - 1,9V}{R_1} = \frac{3,1V}{R_1} = I_2 + I_{B2} = (0,96 + 1,4) \mu A$$

$$= 2,36 \mu A \quad \Rightarrow \quad R_1 = \frac{3,1V}{2,36} = \underline{\underline{1,31 k\Omega}}$$

B4/
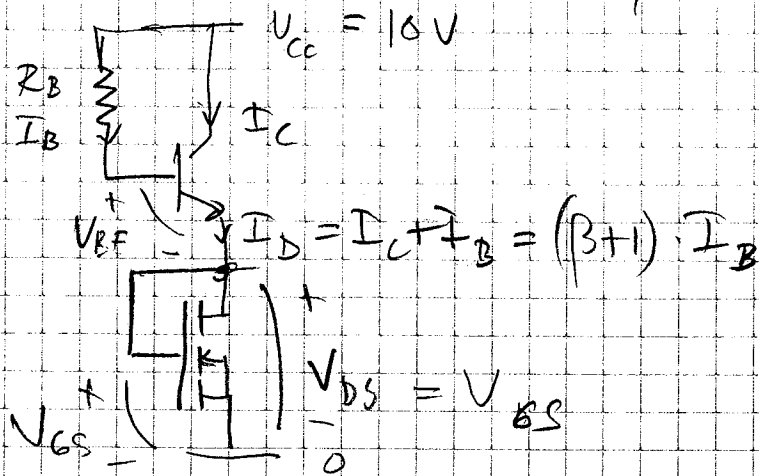
$$K = \frac{1}{2} K_P \frac{W}{L} = \frac{1}{2} \cdot 50 \mu\text{A/V}^2 \frac{100 \mu\text{m}}{10 \mu\text{m}} = 0,25 \text{ mA/V}^2$$



MOS-transistor  
är konstant  
strömgenererbar.

$$I_D = K (V_{GS} - V_{th})^2 = I_B (\beta + 1)$$

$$I_B = \frac{V_{CC} - V_{BE} - V_{DS}}{R_B} = \frac{10 - 0,7 - V_{DS}}{132 \text{ k}\Omega}$$

$$\therefore I_D = 0,25 \mu\text{A/V}^2 (V_{DS} - 2 \text{ V})^2 = \frac{9,3 - V_{DS}}{132 \text{ k}\Omega} \cdot 161$$


$$\Rightarrow (V_{DS} - 2)^2 = \left( \frac{9,3}{33} - \frac{V_{DS}}{33} \right) 161 =$$

$$\Rightarrow V_{DS}^2 - 4V_{DS} + 4 - 45,37 + 4,879V_{DS} = 0$$

$$V_{DS}^2 + 0,879V_{DS} - 41,37 = 0$$

$$V_{DS} = -0,439 \pm \sqrt{0,439^2 + 41,37} = 6,0 \text{ V}$$
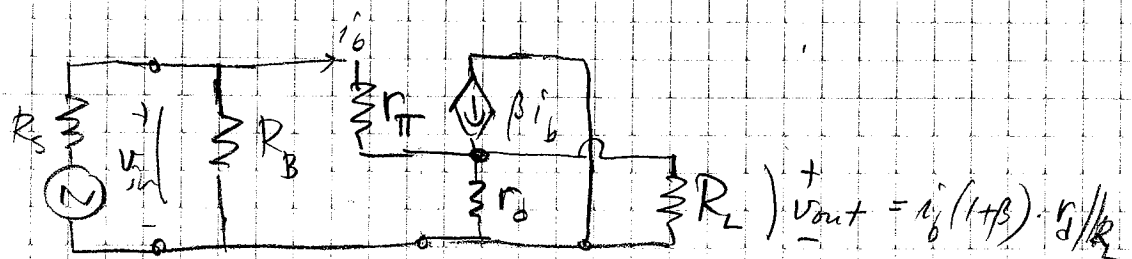
$$I_{DQ} = 4,0 \text{ mA} \approx I_{CQ}$$



$$v_{in} = v_b r_{\pi} + v_{out} = \frac{v_{out}}{(1 + \beta) \beta R_L} r_{\pi} + v_{out}$$

$$\Rightarrow v_{in} = v_{out} \left( 1 + \frac{r_{\pi}}{(1+\beta)(R_2 \parallel R_L)} \right) =$$

$$= v_{out} \cdot \frac{(1+\beta)(R_2 \parallel R_L) + r_{\pi}}{(1+\beta)(R_2 \parallel R_L)}$$

$$\frac{v_{out}}{v_{in}} = \frac{(1+\beta) \cdot (R_2 \parallel R_L)}{r_{\pi} + (1+\beta) \cdot (R_2 \parallel R_L)} = \frac{161 \cdot 20 \text{ k}\Omega \parallel 100 \Omega}{1102 + 161 \cdot 20 \text{ k}\Omega \parallel 100 \Omega}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_{CQ}}{V_T}} = \frac{160}{\frac{4 \text{ mA}}{0,026 \text{ V}}} = 1,04 \text{ k}\Omega$$

$$\Rightarrow A_v = \underline{0,941} \quad \left( A_v = \frac{(1+\beta) \cdot R_2'}{r_{\pi} + (1+\beta) \cdot R_2'} \right.$$

$$Z_o = R_{out} =$$

ent. Formelband.)

$$= \frac{1}{(1+\beta)/(R_2' + r_{\pi}) + \frac{1}{R_2}} = (\text{da } R_2' = R_2 \parallel R_B)$$

$$= \frac{1}{\frac{161}{1,04 \text{ k}\Omega + \frac{20 \cdot 132}{20+132} \text{ k}\Omega} + \frac{1}{20 \text{ k}\Omega}} = 113,7 \approx \underline{114 \Omega}$$

$$A_p = A_v \cdot A_i = \frac{v_{out}}{v_{in}} \cdot \frac{\frac{v_{out}}{R_L}}{\frac{v_{in}}{R_{in}}} = \frac{R_{in}}{R_L} \cdot A_v^2 =$$


$$= \frac{15,1 \text{ k}\Omega}{0,1 \text{ k}\Omega} \cdot 0,941^2 = \underline{133,995}$$

$$R_{in} = R_B \parallel (r_{\pi} + (1+\beta) \cdot R_2') \quad \text{ent. Formelband.}$$

$$\Rightarrow R_{in} = 132 \text{ k}\Omega \parallel (1,04 + (1+160) \cdot 99,5 \Omega) = 132 \text{ k}\Omega \parallel 17 \text{ k}\Omega = 15,1 \text{ k}\Omega$$
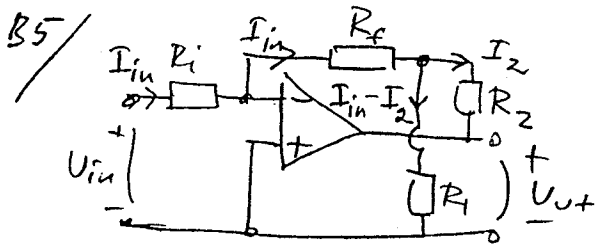
$$R_2' = R_2 \parallel R_L = 20 \text{ k}\Omega \parallel 100 \Omega = 99,5 \Omega$$





Ohms lag

$$I_{in} = \frac{U_{in}}{R_i} \quad \text{--- (1)}$$

Kirch. sp. lag

$$U_{out} + I_2 R_2 - R_1 (I_{in} - I_2) = 0 \quad \text{(2)}$$

$$U_{out} + I_2 R_2 + R_f I_{in} = 0 \quad \text{(3)}$$

(3) ger

$$I_2 = -\frac{1}{R_2} \left( U_{out} + R_f \frac{U_{in}}{R_i} \right)$$

Insättes i (2)

$$U_{out} + (R_1 + R_2) \cdot \frac{1}{-R_2} \left( U_{out} + R_f \frac{U_{in}}{R_i} \right) - R_1 \cdot \frac{U_{in}}{R_i} = 0$$

$$\Rightarrow U_{out} \left( 1 - \frac{R_1}{R_2} - \frac{R_1}{R_2} \right) = U_{in} \left( \frac{R_1}{R_i} + \frac{R_1 + R_2}{R_2} \cdot \frac{R_f}{R_i} \right)$$

$$\Rightarrow A_u = \frac{U_{out}}{U_{in}} = -\frac{R_2}{R_1} \left( \frac{R_1}{R_i} + \frac{R_1}{R_2} \cdot \frac{R_f}{R_i} + \frac{R_f}{R_i} \right) =$$

$$= -\left( \frac{R_2}{R_i} + \frac{R_f}{R_i} + \frac{R_2}{R_1} \cdot \frac{R_f}{R_i} \right)$$