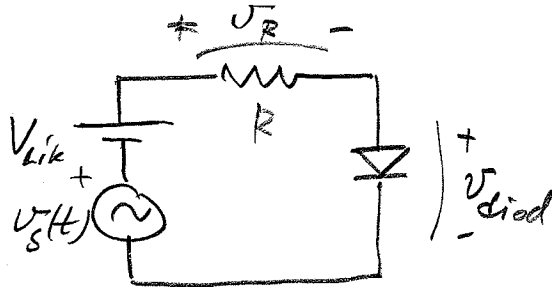


Svar till tenta i Elektronik 5p, E2, T2, D3, 26/10-03

A1.  $A_V = \frac{R_1 + R_2}{R_1} = \frac{100 + 20}{20} = 6,99$

$\Rightarrow A_V = \frac{U_{OUT, max}}{U_{IN, max}} \Rightarrow U_{IN, max} = \frac{\pm 12V}{6} = \underline{\pm 2V}$



A2.



Man mäter signal-spänningarna över diod och motstånd R

$r_d = \frac{U_{diod}}{\frac{U_R}{R}} = \frac{R \cdot U_{diod}}{U_R}$

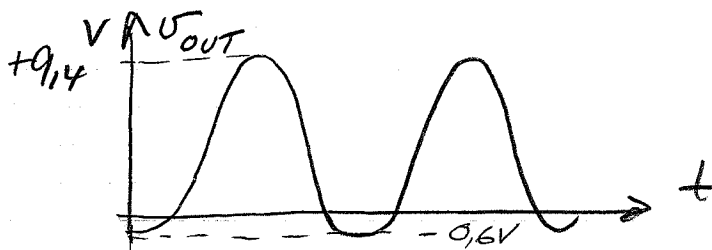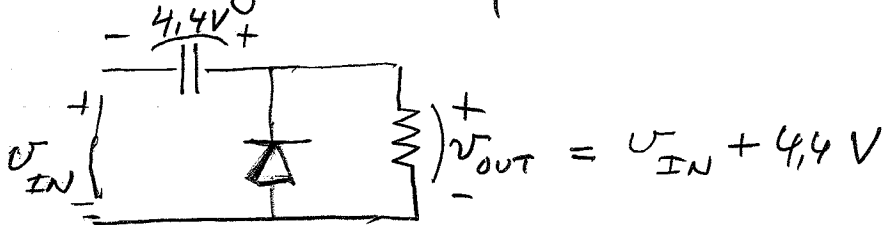
A3. Kondensatorn laddas till  $5 - 0,6 = 4,4V$  under 1:a negativa haloperioden.



A4.  $C = \frac{I_L \cdot T}{V_r} = \frac{20V}{100\Omega} \cdot \frac{20ms}{4V} = 1\mu F = \underline{1000\mu F}$

A5.


$U_{IN} > 5V$

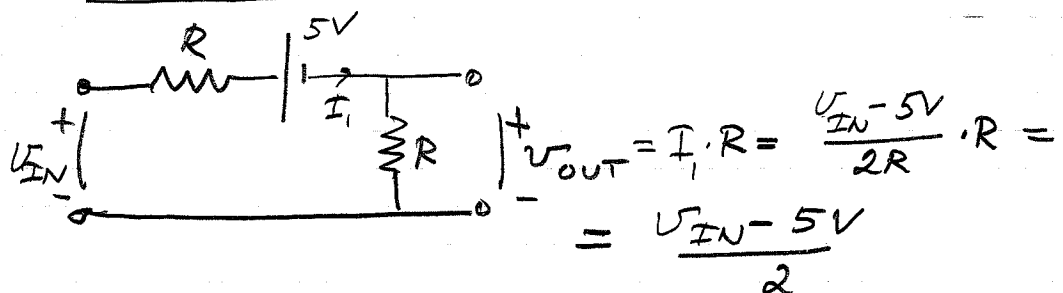


$U_{OUT, max} = \frac{10 - 5}{2} = 2,5V$

forts  
45.


$$V_{IN} < -0,7V$$

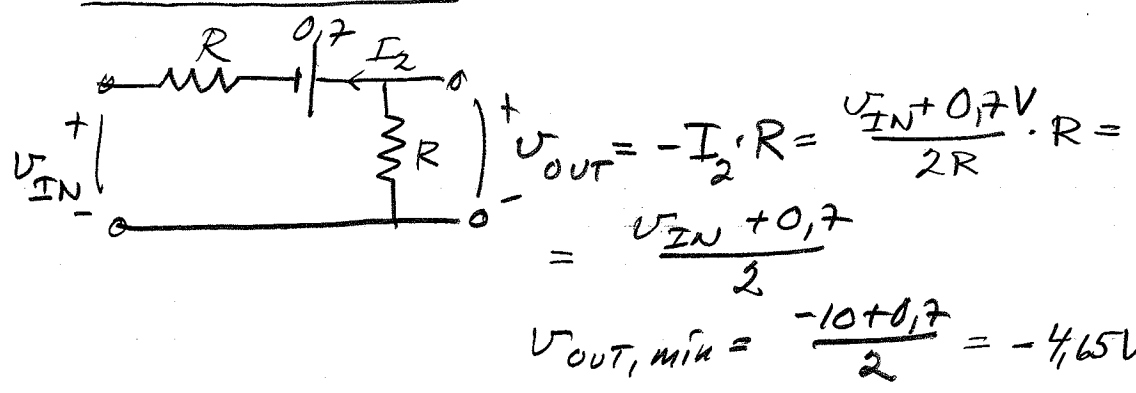

$V_{OUT} = 0$  da  $-0,7V < V_{IN} < 5V$

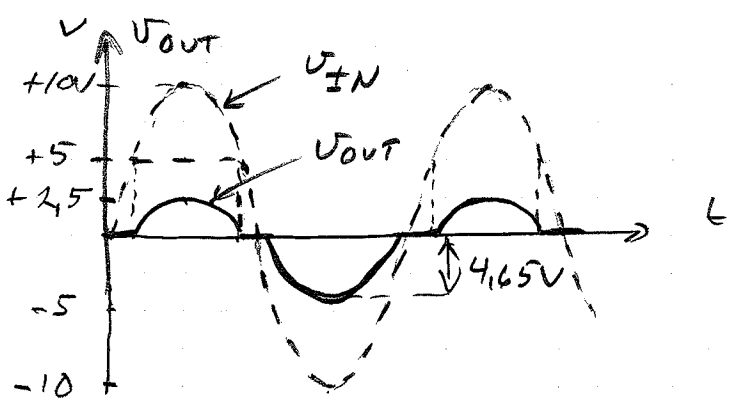

46

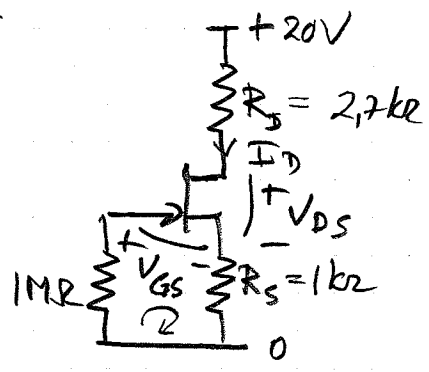

Kirch. spän.lag ger

$$V_{GS} + I_D \cdot R_S = 0$$

$$\Rightarrow V_{GS} = -I_D \cdot 1k\Omega$$


Ritas in i diagrammet  
Skärningen med kurvan  
ger

$$I_{DQ} \approx \underline{3,7mA} \quad (V_{GSQ} = -3,7V)$$


Arbetslinjens ekv. ger

$$20V = V_{DS} + I_D \cdot (R_D + R_S) \Rightarrow V_{DSQ} = 20 - 3,7 \cdot 3,7 = \underline{6,3V}$$

47

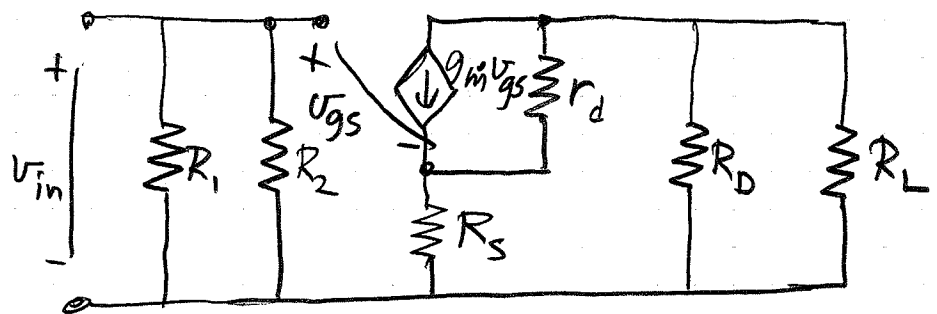


A8. Förstärkarstegets utgång

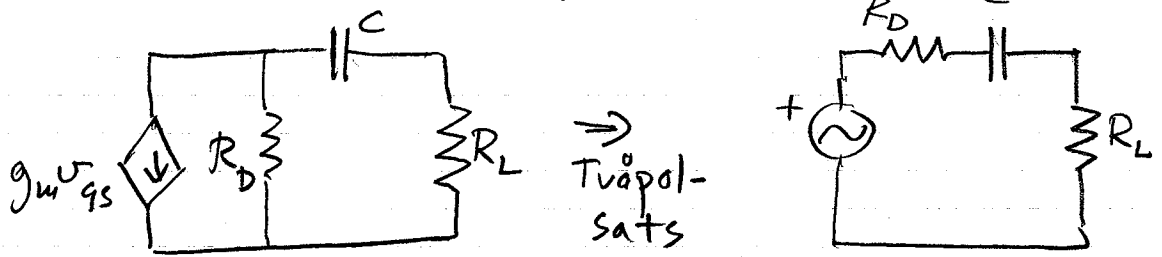

$$f_{ng} = \frac{1}{2\pi(R_D + R_L) \cdot C} = \frac{1}{2\pi \cdot (2+5) \cdot 10^3 \cdot 10^{-5}} = \underline{2,3 \text{ Hz}}$$


A9.

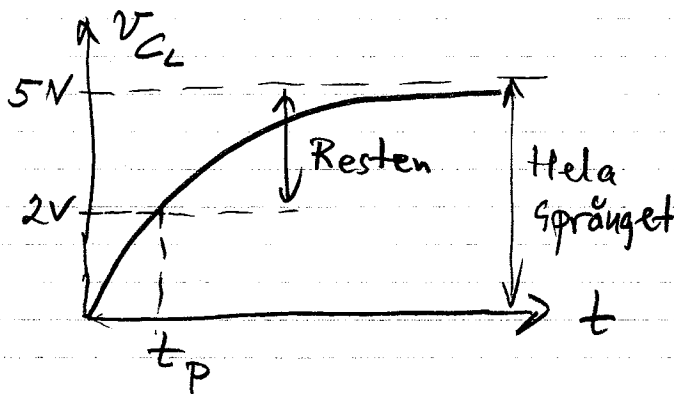

$$t_p = T \ln \frac{\text{Hela språnget}}{\text{Resten}} = R_D C \ln \frac{5V}{3V} = \underline{0,245 \mu s}$$

A10. NOR-grind  $\Rightarrow X = \overline{A+B+C} = (\overline{A} \overline{B} \overline{C})'$

B1.

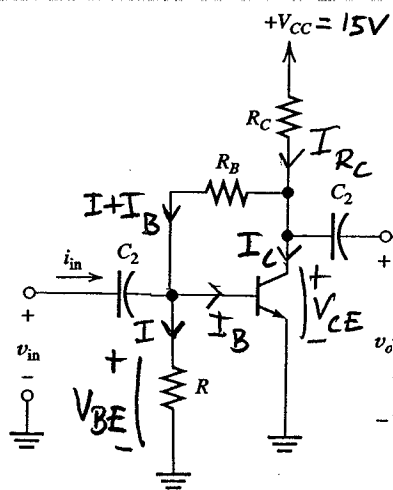

Kirch. strömlag ger

$$I_{RC} = I_C + I + I_B = I + I_B(1+\beta)$$

Ohms lag

$$I = \frac{V_{BE}}{R} = \frac{0,7V}{15k\Omega} = 46,7 \mu A$$

Kirch. spänn. lag ger

$$\begin{cases} V_{CE} = (I + I_B) \cdot R_B + V_{BE} & \dots (1) \\ V_{CC} = I_{RC} \cdot R_C + V_{CE} & \dots (2) \end{cases}$$

$$\begin{aligned} \Rightarrow V_{CC} &= I_{RC} \cdot R_C + (I + I_B) R_B + V_{BE} = \\ &= (I + I_B(1+\beta)) \cdot R_C + I R_B + I_B R_B + V_{BE} \end{aligned}$$

forts.  
B1/

$$\Rightarrow V_{CC} - I R_C - I R_B - V_{BE} = I_B ((1+\beta) \cdot R_C + R_B)$$

$$15V - 46,7 \mu A \cdot (3,3 + 54) k\Omega - 0,7V = I_B (126 \cdot 3,3 k\Omega + 54 k\Omega)$$

$$\Rightarrow I_B = \frac{11,63V}{469,8 k\Omega} = 24,75 \mu A$$

$$I_{CQ} = \beta \cdot I_{BQ} = 125 \cdot 24,75 \mu A = \underline{3,09 mA}$$

$$V_{CE} = (I + I_B) \cdot R_B + V_{BE} = (46,7 + 24,75) \mu A \cdot 54 k\Omega + 0,7V = \underline{4,56 V}$$

B2/

Arbeitsliniens elev.

$$V_{CC} = V_{CE} + I_C (R_C + R_E) \Rightarrow I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E} =$$

$$= \frac{15V - 5,6V}{(4,7 + 0,2) k\Omega} = 1,92 mA$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1,92 mA}{0,026V} = 73,8 mA/V$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{200}{73,8} k\Omega = 2,71 k\Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel r_{\pi} = 50 \parallel 3,9 \parallel 2,71 k\Omega =$$
$$= \underline{1,54 k\Omega}$$

$$R_{out} = r_o \parallel R_C = 100 \parallel 4,7 k\Omega = \underline{4,49 k\Omega}$$

$$A_v = -g_m \cdot (r_o \parallel R_C \parallel R_L) = -73,8 \cdot 3,098 =$$
$$= -228,6 \approx -\underline{229,99}$$

B3.

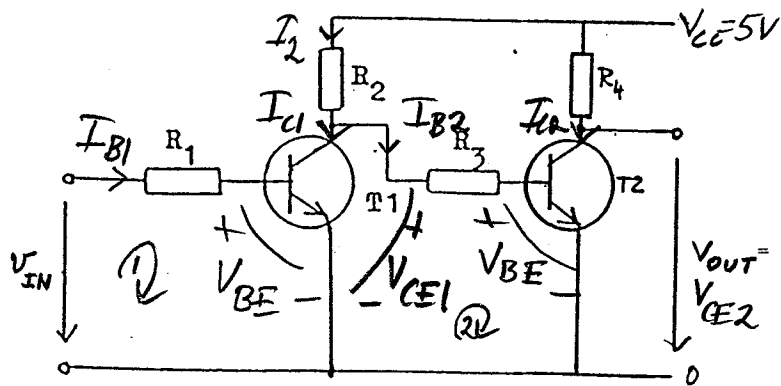

T2 bottnar då  $V_{CE2} = 0,2 V \Rightarrow I_{C2} = \frac{(5-0,2)V}{R_4} = 4,8 \text{ mA}$   
dvs  $I_{B2} \geq \frac{I_{C2}}{\beta} = \frac{4,8 \text{ mA}}{60} = 80 \mu\text{A}$

krävs för att bottna T2

Kirch. spän. lag ger

①  $V_{CE1} = I_{B2} \cdot R_3 + V_{BE} = 80 \mu\text{A} \cdot 20 \text{ k}\Omega + 0,7 \text{ V} = 2,3 \text{ V}$

Kirch. strömlag

$I_{C1} = I_2 - I_{B2} = \frac{V_{CC} - V_{CE1}}{R_2} - I_{B2} = 2,62 \text{ mA}$   
 $\Rightarrow I_{B1} = \frac{I_{C1}}{\beta} = \frac{2,62}{60} \text{ mA} = 43,7 \mu\text{A}$

Kirch. spän. lag ger

②  $V_{IN} = I_{B1} \cdot R_1 + V_{BE} = 43,7 \cdot 20 \text{ mV} + 0,7 \text{ V} = 1,57 \text{ V}$   
 $\therefore V_{IN} \leq 1,57 \text{ V} \Rightarrow$  T2 bottnar

T2 strypt då  $I_{B2} = 0$  dvs  $V_{CE1} \leq 0,7 \text{ V}$   
 $\Rightarrow I_{C1} = \frac{5 \text{ V} - 0,7 \text{ V}}{R_2} = 4,3 \text{ mA} \Rightarrow I_{B1} = \frac{I_{C1}}{\beta} = \frac{4,3 \text{ mA}}{60} = 71,67 \mu\text{A}$


Kirch. spän. lag ger

③  $V_{IN} = I_{B1} \cdot R_1 + V_{BE} = 71,67 \cdot 20 \text{ mV} + 0,7 \text{ V} = 2,13 \text{ V}$   
 $\therefore V_{IN} \geq 2,13 \text{ V} \Rightarrow$  T2 är strypt

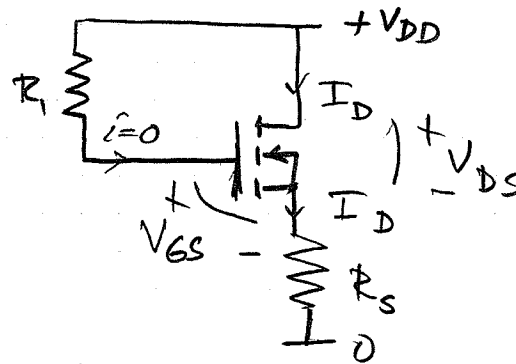84.

$$K = \frac{1}{2} \cdot K_P \cdot \frac{W}{L} = \frac{1}{2} \cdot 40 \cdot \frac{400}{10} = 0,8 \text{ mA/V}^2$$

$$I_D = K(V_{GS} - V_{to})^2 \quad \text{i konst. strömmområdet}$$



$$V_{GS} = V_{DS}$$

Kirch. spän. lag

$$V_{DD} = V_{GS} + I_D \cdot R_S$$

$$\Rightarrow I_D = \frac{V_{DD} - V_{GS}}{R_S}$$

sätt ekv. lika

$$\frac{V_{DD} - V_{GS}}{R_S} = K(V_{GS} - V_{to})^2 = I_D$$

$$\Rightarrow \frac{15V - V_{GS}}{2,5k\Omega} = 0,8 \text{ mA/V}^2 (V_{GS} - 2V)^2$$

$$\Rightarrow \frac{15V - V_{GS}}{2} = V_{GS}^2 - 4V_{GS} + 4$$

$$\Rightarrow V_{GS}^2 - 3,5V_{GS} - 3,5 = 0$$


$$\Rightarrow V_{GS} = \frac{3,5}{2} (\pm) \sqrt{\left(\frac{3,5}{2}\right)^2 + 3,5} = 4,31 \text{ V}$$

$$\Rightarrow I_{DQ} = \frac{(15 - 4,31)V}{2,5k\Omega} = \underline{\underline{4,28 \text{ mA}}}$$

$$V_{DSQ} = V_{DD} - I_{DQ} \cdot R_S = 15 - 4,28 \cdot 2,5 = \underline{\underline{4,31 \text{ V}}}$$

$$g_m = 2 \sqrt{I_{DQ} \cdot K} = 2 \sqrt{4,28 \cdot 0,8} = 3,7 \text{ mA/V}$$

Ekvivalent signalschema

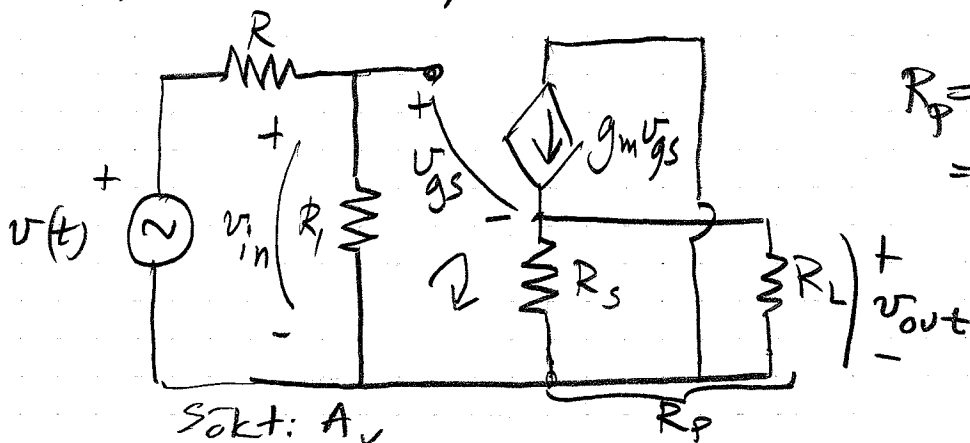

$$R_p = R_S \parallel R_L = 2k\Omega$$

Sökt:  $A_v$

forts  
B4 /

Kirch. spän. lag


$$\mathcal{R} \quad v_{in} - v_{gs} - v_{out} = 0 \Rightarrow v_{gs} = v_{in} - v_{out}$$

Ohms lag

$$v_{out} = g_m v_{gs} \cdot R_p = g_m (v_{in} - v_{out}) \cdot R_p$$

$$\Rightarrow v_{out} (1 + g_m R_p) = g_m v_{in} R_p \Rightarrow A_v = \frac{g_m R_p}{1 + g_m R_p} =$$
$$= \frac{3,7 \cdot 2}{1 + 3,7 \cdot 2} = \underline{\underline{0,8899}}$$
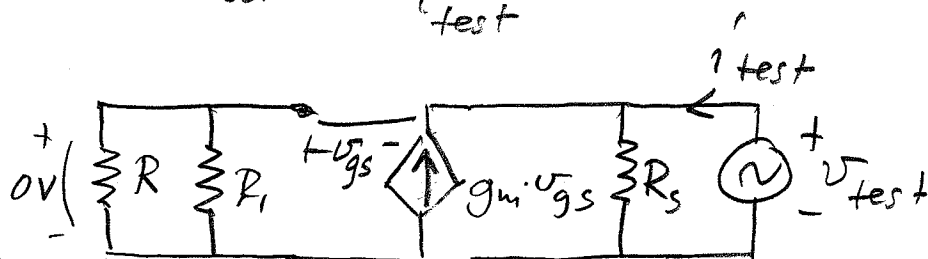
$$\text{Søkt } i_{R_{out}} = \frac{v_{test}}{i_{test}}$$



$$v_{gs} = -v_{test}$$

Kirch. strömlag

$$g_m v_{gs} + i_{test} = \frac{v_{test}}{R_s}$$


}  $\Rightarrow$

$$\Rightarrow -g_m v_{test} + i_{test} = \frac{v_{test}}{R_s}$$

$$\Rightarrow \frac{1}{R_{out}} = \frac{i_{test}}{v_{test}} = g_m + \frac{1}{R_s} = 4,1 \text{ mA/V}$$

$$\Rightarrow R_{out} = \underline{\underline{244 \Omega}}$$

B5.

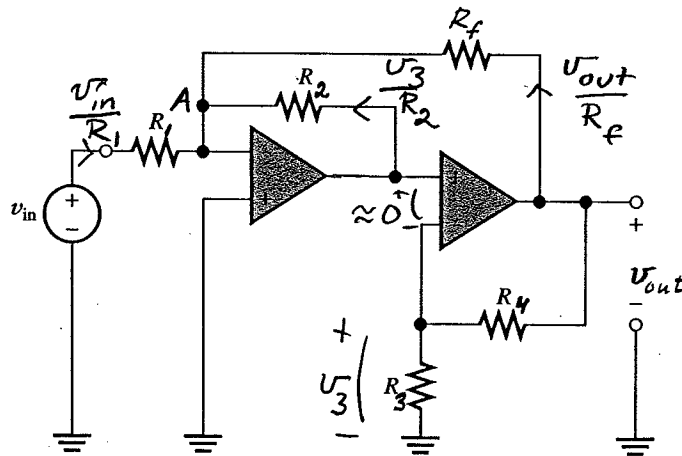

Kirch. strömlag i A ger

$$\frac{v_{in}}{R_1} + \frac{v_3}{R_2} + \frac{v_{out}}{R_f} = 0$$

Spän. delning på utgången ger

$$v_3 = v_{out} \cdot \frac{R_3}{R_3 + R_4}$$

Insattes i ekv. ovan

$$\frac{v_{in}}{R_1} + v_{out} \frac{R_3}{R_2(R_3 + R_4)} + \frac{v_{out}}{R_f} = 0$$

$$\Rightarrow v_{out} \left( \frac{R_3}{R_2(R_3 + R_4)} + \frac{1}{R_f} \right) = - \frac{v_{in}}{R_1}$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = - \frac{1}{R_1 \left( \frac{R_3}{R_2(R_3 + R_4)} + \frac{1}{R_f} \right)} =$$

$$= - \frac{R_2(R_3 + R_4) \cdot R_f}{R_1(R_3 R_f + R_2 R_3 + R_2 R_4)}$$