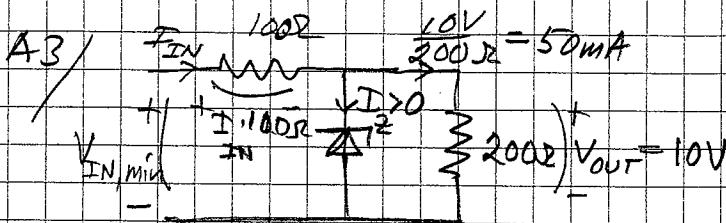


Tenta månd. 16/8-09, Elektronik Ak.

- A1/ Efter pol 1 - -20dB/Åkead  
 " pol 2 - -40dB/Åkead  
 " pol 3 - -60dB/Åkead


A2/ ang  $\beta_A = 0$  och  $\beta_A = 1$



$$I_{ZN} > 50 \text{ mA}$$

$$V_{IN, \text{min}} = 50 \text{ mA} \cdot 100 \Omega + 10 \text{ V} = 15 \text{ V}$$

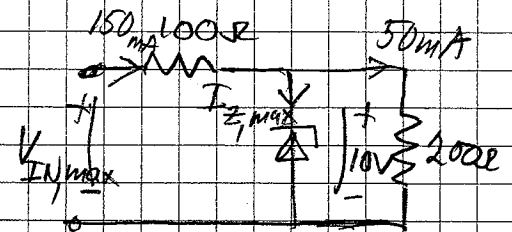
$$\therefore V_{\text{rippel}} = 5 \text{ V}$$



$$I_{Z, \text{max}} = \frac{1 \text{ W}}{10 \text{ V}} = 100 \text{ mA}$$

$$\therefore V_{IN, \text{max}} = 150 \text{ mA} \cdot 100 \Omega + 10 \text{ V} = 25 \text{ V}$$

A4/

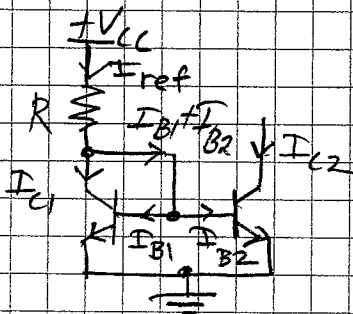

$$I_{\text{ref}} = I_{C1} + I_{B1} + I_{B2}$$

Transistorerna lika


$$I_{C1} = I_{C2} \text{ och } I_{B1} = I_{B2}$$

$$\Rightarrow I_{\text{ref}} = \beta \cdot I_{B1} + I_{B1} + I_{B1} = (\beta + 2) \cdot I_{B1} = \frac{V_{cc} - V_{BE}}{R} =$$


$$= \frac{5 \text{ V} - 0,7 \text{ V}}{12 \text{ k}\Omega} = \frac{4,3 \text{ V}}{12 \text{ k}\Omega}$$

$$\Rightarrow I_{C2} = \frac{\beta}{\beta + 2} \cdot \frac{4,3 \text{ V}}{12 \text{ k}\Omega} = 0,3445 \text{ mA}$$

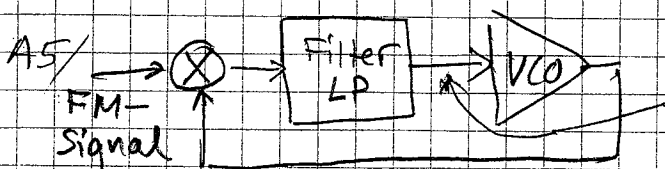då  $\beta = 50$  och  $0,3583 \text{ mA}$  då  $\beta \rightarrow \infty$  " skiltnad  $0,014 \text{ mA}$



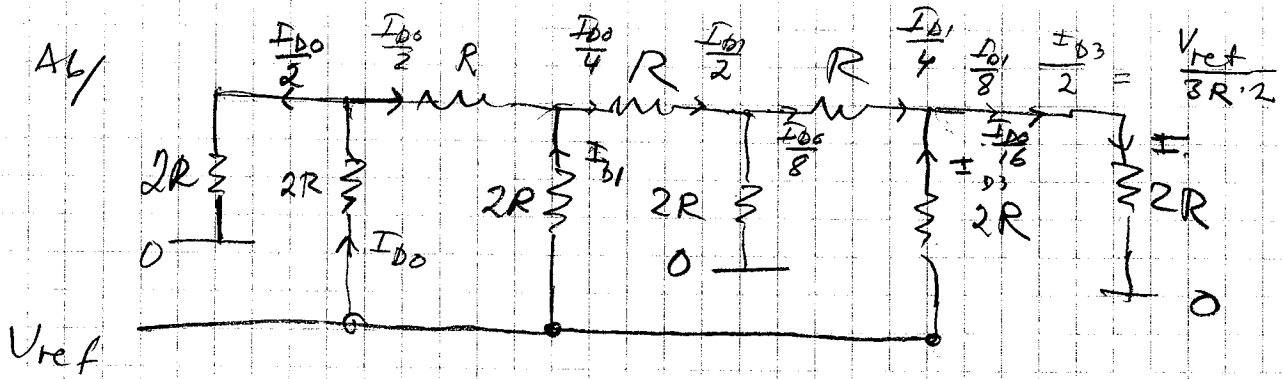Lågfrekventa signalen från LP-filtret ändrar VCO:s frekvens i takt med FM-signalen.



$$I = \frac{I_{D3}}{2} + \frac{I_{D1}}{8} + \frac{I_{D0}}{16} = \frac{V_{ref}}{3R} \left( \frac{1}{2} + \frac{1}{8} + \frac{1}{16} \right)$$

$$I_{D0} = I_{D1} = I_{D3} = \frac{V_{ref}}{3R}$$

$$V_{in} = I \cdot 2R = \frac{V_{ref} \cdot 2R}{3R} \left( \frac{1}{2} + \frac{1}{8} + \frac{1}{16} \right) =$$

$$= \frac{10 \cdot 2}{3} \left( \frac{1}{2} + \frac{1}{8} + \frac{1}{16} \right) = \underline{\underline{4,58 V}}$$

A7/

$$f_{ng} = \frac{1}{2\pi C \cdot R_1} = \frac{1}{2\pi \cdot 120 \cdot 10^{-9} \cdot 56 \cdot 10^3} = \underline{\underline{23,7 Hz}}$$

A8/

$$C_p = 12,000 \mu F \quad f_s = 5,000 MHz, \quad R_s = 50 \Omega$$

$$Q = 20000 \quad \text{Solut: } f_p$$

$$f_p = \frac{1}{2\pi \sqrt{C_{eq} L_s}}$$

$$= \frac{50 \cdot 20000}{2\pi \cdot 5 \cdot 10^6}$$

$$Q = \frac{\omega_s L_s}{R_s} \Rightarrow L_s = \frac{R_s \cdot Q}{\omega_s} =$$


$$\left\{ \begin{aligned} \frac{1}{C_{eq}} &= \frac{1}{C_s} + \frac{1}{C_p} = \omega_s^2 L_s + \frac{1}{C_p} \\ \omega_s^2 &= \frac{1}{L_s \cdot C_s} \Rightarrow C_s = \frac{1}{\omega_s^2 \cdot L_s} \end{aligned} \right.$$

$$f_p = \frac{1}{2\pi \sqrt{\frac{1}{\omega_s^2 L_s + \frac{1}{C_p}} \cdot L_s}} = \frac{1}{2\pi} \cdot \frac{\sqrt{\omega_s^2 L_s + \frac{1}{C_p}}}{L_s} =$$

$$= \frac{1}{2\pi} \cdot \sqrt{\omega_s^2 + \frac{1}{L_s C_p}} = \frac{1}{2\pi} \sqrt{\omega_s^2 + \frac{\omega_s}{R_s Q \cdot C_p}}$$

$$= \frac{1}{2\pi} \sqrt{(2\pi \cdot 5 \cdot 10^6)^2 + \frac{2\pi \cdot 5 \cdot 10^6}{50 \cdot 20000 \cdot 12 \cdot 10^{-6}}} = \underline{\underline{5,0066 MHz}}$$


A9 /

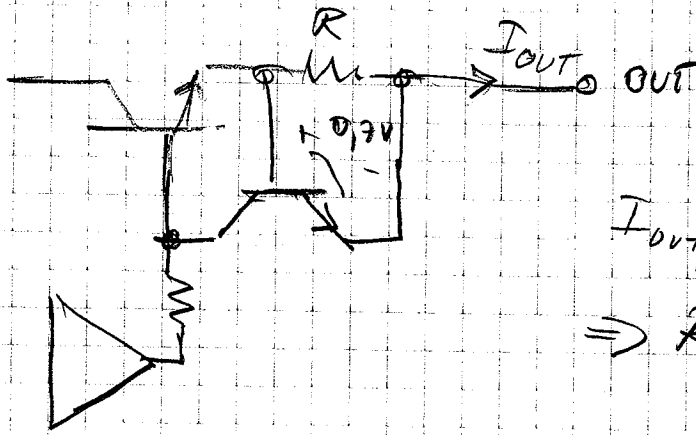

$$I_{out, max} = \frac{0,7V}{R} = 2A$$

$$\Rightarrow R = \underline{\underline{0,35\Omega}}$$

A10 /

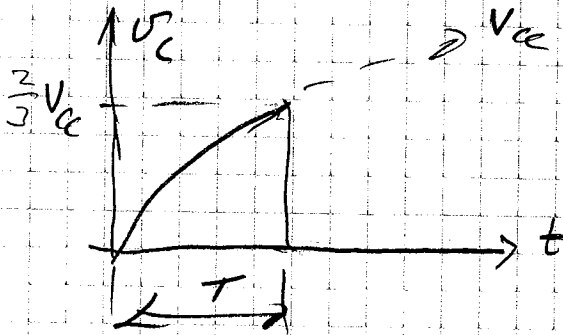

$$t = \tau \ln \frac{A}{B}$$


per

$$T = R_A \cdot C \ln \frac{V_{cc}}{\frac{1}{3} V_{cc}}$$

$$= 12 \cdot 10^3 \cdot 10 \cdot 10^{-9} \ln 3 =$$

$$= \underline{\underline{0,132 \text{ ms}}}$$

B1/

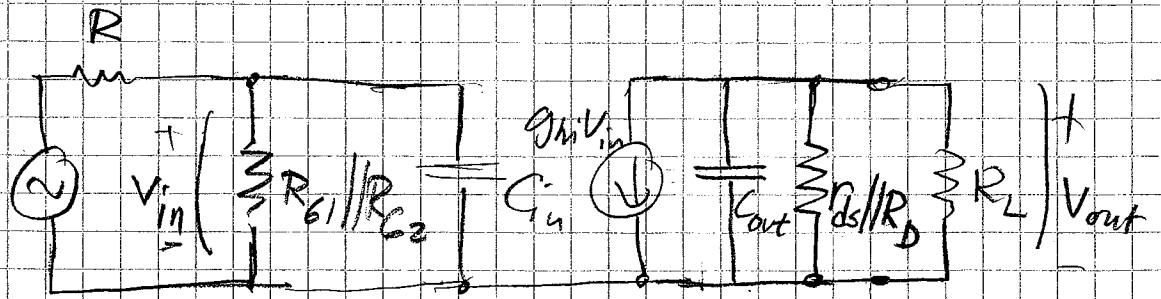

$$\begin{cases} C_{in} = C_{gs} + (1 - A_v) \cdot C_{gd} \\ C_{out} = C_{ds} + \frac{A_v - 1}{A_v} \cdot C_{gd} \end{cases}$$

$$g_m = 2\sqrt{I_{DQ}} \cdot K \quad A_v = -g_m \cdot (R_D \parallel R_{ds} \parallel R_L)$$

$$f_{ag, in} = \frac{1}{2\pi (R_{G1} \parallel R_{G2} \parallel R) \cdot C_{in}}$$

$$f_{ag, out} = \frac{1}{2\pi (R_D \parallel R_{ds} \parallel R_L) \cdot C_{out}}$$

$$g_m = 2 \sqrt{2,2 \cdot \frac{8}{2,5^2}} = \frac{2}{2,5} \sqrt{22 \cdot 8} = 3,356 \text{ mA/V}$$

$$K = \frac{I_{DSS}}{V_{to}^2} = \frac{8}{2,5^2}$$

$$R_D \parallel R_{ds} \parallel R_L = 5 \parallel 100 \parallel 12 = 3,409 \text{ k}\Omega$$

$$A_v = -3,356 \cdot 3,409 = -11,4499 \text{ V}$$

$$C_{in} = 3,5 + (11,44 + 1) \cdot 1 = 15,94 \text{ pF}$$

$$R_{G1} \parallel R_{G2} \parallel R = 1,5 \text{ M}\Omega \parallel 0,68 \text{ M}\Omega \parallel 100 \text{ k}\Omega = 82,39 \text{ k}\Omega$$

$$f_{ag, in} = \frac{1}{2\pi \cdot 82,39 \cdot 10^3 \cdot 15,94 \cdot 10^{-12}} = 121,2 \text{ kHz}$$

forts  
B1

$$r_{ds} // R_D // R_L = 180 \text{ k}\Omega // 5 \text{ k}\Omega // 12 \text{ k}\Omega = 3,41 \text{ k}\Omega$$

$$C_{out} = C_{ds} + C_{gd} \frac{A_v - 1}{A_v} = 1,2 + \frac{-11,44 - 1}{-11,44} \cdot 1$$

$$= 2,2874 \text{ pF}$$

$$f_{eq,out} = \frac{1}{2\pi \cdot 3,41 \cdot 10^3 \cdot 2,287 \cdot 10^{-12}} =$$

$$= \underline{20,4 \text{ MHz}}$$

$$\frac{1}{f_{eq,tot}} = \frac{1}{f_{eq,fn}} + \frac{1}{f_{eq,out}} = \frac{1}{121,2 \text{ kHz}} + \frac{1}{20,4 \text{ MHz}}$$

$$f_{eq,tot} = \underline{120,5 \text{ kHz}}$$

B2)

$$\frac{V_{out}}{U_{in}} = - \frac{R_2}{R_3 // (R_1 + j\omega C)}$$

$$= - \frac{R_2}{\frac{R_3 (R_1 + j\omega C)}{R_3 + R_1 + j\omega C}} = - \frac{R_2 (R_1 + j\omega C)}{R_3 (R_1 + j\omega C)}$$

$$= - \frac{R_2 (1 + j\omega C (R_1 + R_3))}{R_3 (1 + j\omega C \cdot R_1)}$$

$$f_p = \frac{1}{2\pi C R_1} \quad \text{ar pol} \quad f_p = 4,42 \cdot 10^3 \text{ Hz}$$


$$f_n = \frac{1}{2\pi C (R_1 + R_2)} \quad \text{ar nullstelle}$$

$$f_n = \frac{1}{2\pi \cdot 20 \cdot 10^{-9} \cdot 19,8 \cdot 10^3} = \underline{402 \text{ Hz}}$$

70113  
B2/

$$|A_v|_{f \rightarrow 0} = \frac{R_2}{R_3} = \frac{100}{18} = 5,56 \text{ 99r}$$

$$|A_v|_{f \rightarrow \infty} = \frac{R_2}{2,1 R_3} = \frac{100}{1,8 // 18} = 6,11 \text{ 99r}$$

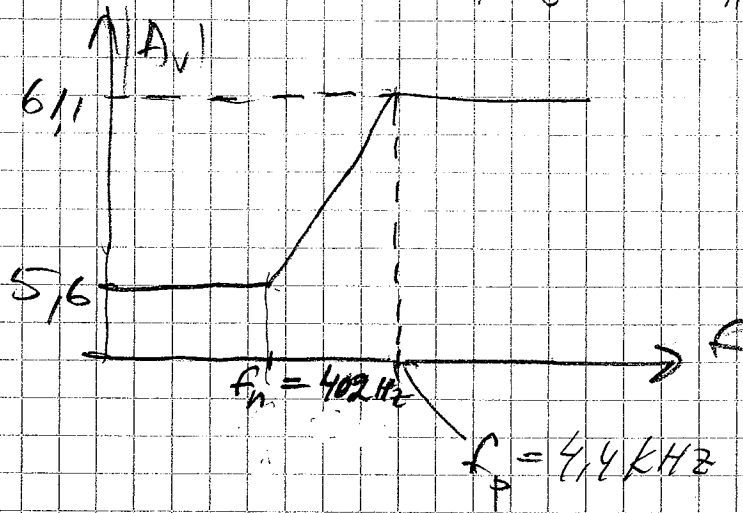

B3/ Dia ordningens LP-filtr

$$A_v = \frac{\omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2} \quad \omega_0 = \frac{1}{\sqrt{2 R_2 C_2}}$$

$$Q = \frac{\sqrt{R_1 R_2 C_1}}{\sqrt{C_2} (R_1 + R_2)}$$

Poler:

$$s_{1,2} = -\frac{\omega_0}{2Q} \pm \sqrt{\left(\frac{\omega_0}{2Q}\right)^2 - \omega_0^2}$$

$$\therefore \frac{\omega_0}{2Q} = 5 \cdot 10^3 \text{ och } \omega_0^2 = \left(\frac{\omega_0}{2Q}\right)^2 = (4 \cdot 10^3)^2$$

$$\Rightarrow \omega_0^2 = (4 \cdot 10^3)^2 + (5 \cdot 10^3)^2 \Rightarrow \omega_0 = 6,4 \cdot 10^3 \text{ rad/s}$$

$$\therefore \frac{6,4 \cdot 10^3}{2 \cdot 5 \cdot 10^3} = Q = 0,64$$

$$Q = \frac{R \sqrt{C_1}}{\sqrt{C_2} \cdot 2R} = 0,64$$

$$C_1 = C_2 \cdot 1,28^2$$

$$\omega_0 = \frac{1}{R \sqrt{C_2}} = 6,4 \cdot 10^3$$

$$\Rightarrow C_1, C_2 = \left(\frac{1}{12 \cdot 6,4 \cdot 10^6}\right)^2$$


Ant  
B3

$$C_2 \cdot 1,28^2 \cdot C_2 = \left( \frac{1}{12,64 \cdot 10^6} \right)^2$$

$$C_2 = \frac{10^{-6}}{1,28 \cdot 12,64} = \underline{\underline{10,2 \text{ nF}}}$$

$$C_1 = C_2 \cdot 1,28^2 = 10,2 \cdot 1,28^2 = \underline{\underline{16,7 \text{ nF}}}$$

B4

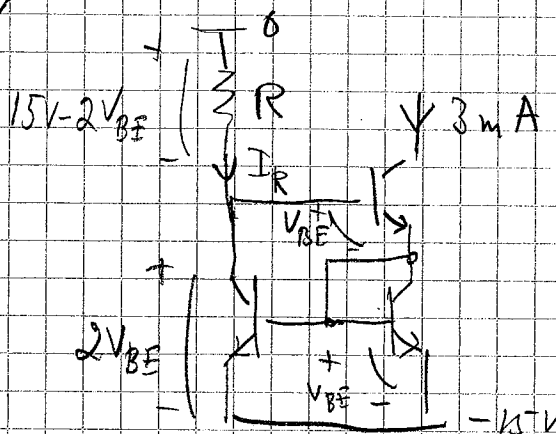

$\beta$  stor  $\Rightarrow$

$$3 \text{ mA} = \frac{15 \text{ V} - 2 \cdot 0,7}{R}$$

$$R = \frac{13,6}{3} = \underline{\underline{4,53 \text{ k}\Omega}}$$

Branch for  $Q_3$  och  $Q_4$

$$g_m = \frac{I_{CG}}{V_T} = \frac{1,5 \text{ mA}}{0,026 \text{ V}} = 57,69 \text{ mA/V}$$

$$V_{out1} = -\frac{1}{2} g_m \cdot R_D (v_{in1} - v_{in2})$$

$$V_{out2} = +\frac{1}{2} g_m (R_D \parallel R_L) \cdot (v_{in1} - v_{in2})$$

$$A_{vdb} = \frac{V_{out1} - V_{out2}}{v_{in1} - v_{in2}} = \frac{-\frac{1}{2} g_m (R_D + R_D \parallel R_L) \cdot (v_{in1} - v_{in2})}{v_{in1} - v_{in2}}$$

$$= -\frac{1}{2} g_m (R_D + R_D \parallel R_L) = -\frac{1}{2} 57,69 \cdot \left( 10 + \frac{10 \cdot 20}{30} \right) =$$

$$= \underline{\underline{-481 \text{ ggr}}}$$


$$CMRR_s = \frac{r_{\pi} + (\beta+1) \cdot (R_{EF} + 2R_{EB})}{r_{\pi} + (\beta+1) R_{EF}}$$

$$R_{EF} = 0 \quad R_{EB} = 2 \cdot r_o \quad r_{\pi} = \frac{\beta}{g_m} = \frac{250}{57,69} = 4,33 \text{ k}\Omega$$

fortz  
B4/

$$CMRR_5 = \frac{4,33 \text{ k}\Omega + 251 \cdot 2 \cdot 2 \cdot 150 \text{ k}\Omega}{4,33 \text{ k}\Omega + 0}$$
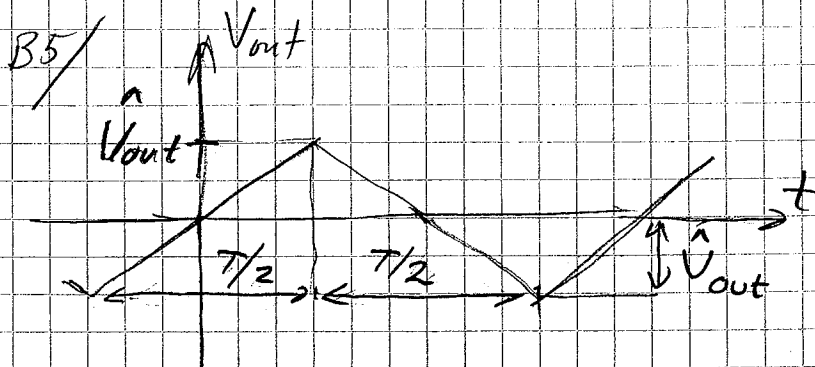
$$= 3,48 \cdot 10^4 = \underline{34,8 \cdot 10^3 \text{ ggr}} \quad (90,8 \text{ dB})$$




Integratorns utspänning

$$v_{out} = \pm \frac{1}{R_3 C} \int_0^t v_{in} dt = \pm \frac{1}{R_3 C} v_{out, \max} t$$

$$\hat{v}_{out} = \frac{1}{R_3 C} v_{out, \max} \cdot \frac{T}{2} =$$
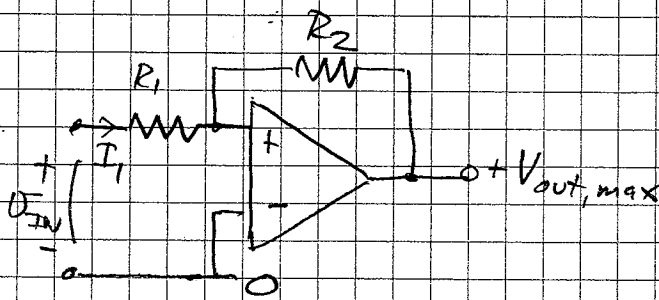
$$= \frac{1}{15 \cdot 10^3 \cdot 33 \cdot 10^{-9}} \cdot 10 \text{ V} \cdot \frac{T}{2}$$



Omslag då  $v_i = 0$

$$I_1 = \frac{v_{IN}}{R_1} = -\frac{v_{out, \max}}{R_2}$$

$$\Rightarrow v_{IN} = -\frac{R_1}{R_2} v_{out, \max}$$

$$= -\frac{10}{27} \cdot 10 = \underline{-3,7 \text{ V}}$$

Om utspänning är  $-v_{out, \max}$

får omslag då  $v_{IN} = +3,7 \text{ V}$

$$\Rightarrow \hat{v}_{out} = 3,7 \text{ V} = \frac{1}{15 \cdot 10^3 \cdot 33 \cdot 10^{-9}} \cdot 10 \text{ V} \cdot \frac{T}{2}$$

$$\Rightarrow T = 3,67 \cdot 10^{-4} \text{ s} \Rightarrow f = \frac{1}{T} = \underline{2,73 \text{ kHz}}$$