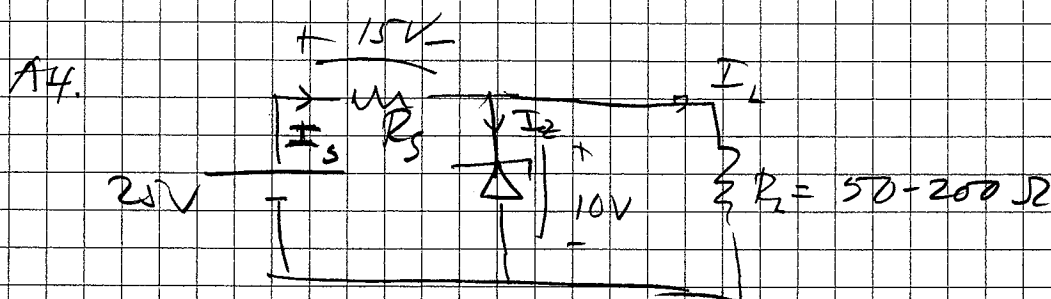


Tenta Elektronik Sk. 17/4-2004

A1. Tvin pol 2, 20dB/dekad mellan Pol 1 och 2  
 $\Rightarrow$  motkopplingen sänker  $|A_v|$  med 20dB

A2.  $\beta A < 1$  vid  $\arg \beta A = 180^\circ$

A3.  $V_{out,rippel} = V_{rippel} \frac{25\Omega}{25\Omega + 1200\Omega} \Rightarrow \frac{V_{out,rippel}}{V_{rippel}} = \frac{25}{1225} \Rightarrow -33,8dB$



$$\left\{ \begin{array}{l} I_{Z,max} \text{ då } R_L = 200\Omega \Rightarrow I_L = \frac{15V}{200} = 0,075A \\ I_{Z,max} = \frac{2W}{10V} = 0,2A \end{array} \right.$$

$$\Rightarrow I_S = 0,275A \Rightarrow R_S = \frac{15V}{0,275A} = 54,5\Omega$$

$R_S \geq 60\Omega$  annars blir  $I_Z$  för stor.

$$\text{Antag } R_L = 50\Omega \Rightarrow I_L = \frac{15V}{50} = 0,3A$$

$$\text{och } I_Z \geq 0 \Rightarrow R_S = \frac{15V}{0,2A} = 75\Omega$$

$$\therefore \underline{\underline{60 \leq R_S \leq 75\Omega}}$$

A5.  $f_{out} = f_r \cdot \frac{M}{N}$

A6.  $\frac{6,25}{10} \cdot 256 = 160$  dvs räknaman står på 010100000

A7/

$$R_2 \approx \frac{V_T}{I_{C2}} \cdot \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$

$$I_{C1} = \frac{V_{CC} - V_{BE1}}{R_1} = \frac{10 - 0,7}{R_1}$$

$$I_{C2} = I = 10 \mu\text{A}$$

$$\therefore 14 \cdot 10^3 \approx \frac{0,026}{10 \cdot 10^{-6}} \ln x$$

$$\frac{14 \cdot 10^3 \cdot 10^{-5}}{0,026} = \ln x \Rightarrow x = 218 = \frac{9,3}{R_1 \cdot 10^{-5}}$$


$$= 5385$$

$$\Rightarrow R_1 = \frac{9,3}{218 \cdot 10^{-5}} = \underline{\underline{4,27 \text{ k}\Omega}}$$

A8/

$$f_{0q} = \frac{1}{2\pi \cdot 120 \cdot 10^{-12} \cdot 33 \cdot 10^3} = \underline{\underline{40,2 \text{ kHz}}}$$

A9/

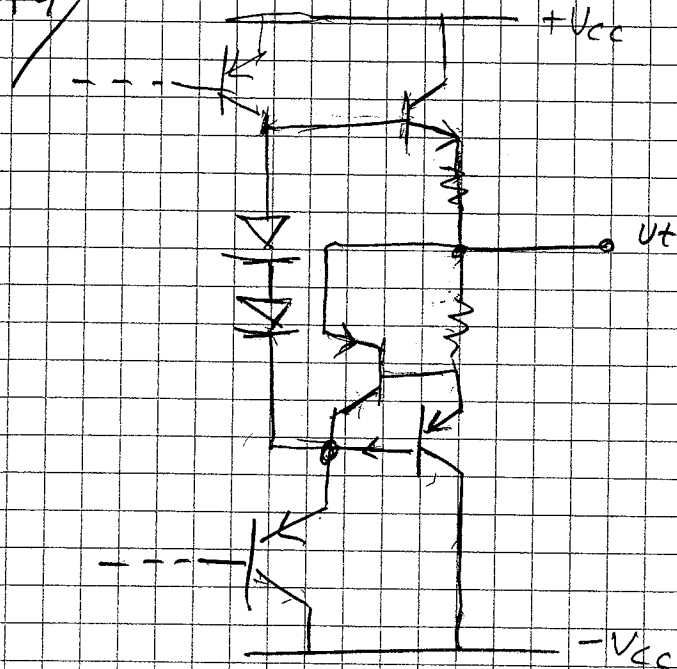


A10/

$$\frac{1}{C_{eq}} = \frac{1}{C_S} + \frac{1}{C_P} = \frac{1}{25 \cdot 10^{-15}} + \frac{1}{6 \cdot 10^{-12}} \Rightarrow C_{eq} = 2,4886 \cdot 10^{-14} \text{ F}$$

$$f_p = \frac{1}{2\pi \sqrt{C_{eq} \cdot L_S}} = 10 \cdot 10^6 \text{ Hz} \Rightarrow \frac{1}{(2\pi \cdot 10^6)^2 \cdot C_{eq}} = L_S =$$

$$\approx 0,01017 \text{ H} \quad f_s = \frac{1}{2\pi \sqrt{L_S \cdot C_S}} = \frac{1}{2\pi \sqrt{0,01017 \cdot 25 \cdot 10^{-5}}} = \underline{\underline{9,98136 \text{ MHz}}}$$

B1/

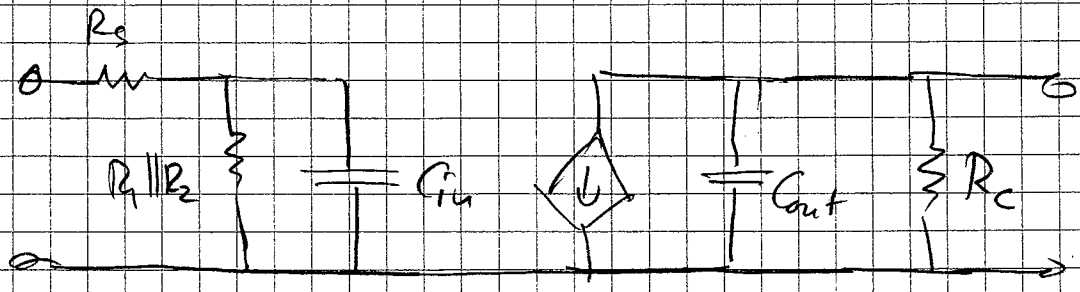

$$C_{in} = C_{gs} + (1 - A_v) \cdot C_{gd}$$

$$C_{out} = C_{ds} + \frac{A_v - 1}{A_v} \cdot C_{gd}$$

$$A_v = -g_m R_c = -2,5 \cdot 15 = -37,5 \text{ ggr}$$

$$C_{in} = 1,8 + (1 + 37,5) \cdot 0,5 = 21,05 \text{ pF}$$

$$C_{out} = 0,6 + \frac{-37,5 - 1}{-37,5} \cdot 0,5 = 1,113 \text{ pF}$$

$$f_{og, in} = \frac{1}{2\pi (R_s \parallel R_1 \parallel R_2) \cdot C_{in}} = \frac{1}{2\pi \cdot 505 \cdot 10^3 \cdot 21,05 \cdot 10^{-12}}$$

$$\left(1 \parallel \frac{12 \cdot 4,8}{12 + 4,8}\right) = 505 \text{ k}\Omega$$

$$= \underline{14,97 \text{ kHz}}$$

$$f_{og, out} = \frac{1}{2\pi R_c \cdot C_{out}} = \frac{1}{2\pi \cdot 15 \cdot 10^3 \cdot 1,113 \cdot 10^{-12}}$$

$$= \underline{9,53 \text{ MHz}}$$

$$\frac{1}{f_{og, tot}} = \frac{1}{f_{og, in}} + \frac{1}{f_{og, out}} \Rightarrow f_{og, tot} = \underline{14,95 \text{ kHz}}$$


$$\begin{aligned}
 B2/ \quad A_u &= - \frac{10R // \left(\frac{1}{sC} + R\right)}{\frac{R}{10}} = - \frac{10 \cdot \frac{10R(R + \frac{1}{sC})}{10R + R + \frac{1}{sC}}}{R} \\
 &= - \frac{100R(R + \frac{1}{sC})}{R(11R + \frac{1}{sC})} \cdot \frac{s}{s} = - \frac{100(sR + \frac{1}{C}) \cdot R}{(11R \cdot s + \frac{1}{C}) \cdot 11R} \\
 &= - \frac{100(s + \frac{1}{RC}) \cdot R}{(s + \frac{1}{11R \cdot C}) \cdot 11R}
 \end{aligned}$$

$$\begin{aligned}
 \text{Nullstelle} \quad f_0 &= \frac{1}{2\pi RC} = \frac{1}{2\pi \cdot 18 \cdot 10^3 \cdot 20 \cdot 10^{-9}} \\
 &= \underline{442 \text{ Hz}}
 \end{aligned}$$

$$\text{Pol} \quad f_p = \frac{1}{2\pi 11RC} = \underline{41,2 \text{ Hz}}$$

$$\begin{aligned}
 f \rightarrow \infty \Rightarrow A_u &= - \frac{R // 10R}{\frac{R}{10}} = - \frac{10 \cdot \frac{R \cdot 10R}{11R}}{R} \\
 &= - \frac{100}{11} = \underline{-9,09}
 \end{aligned}$$
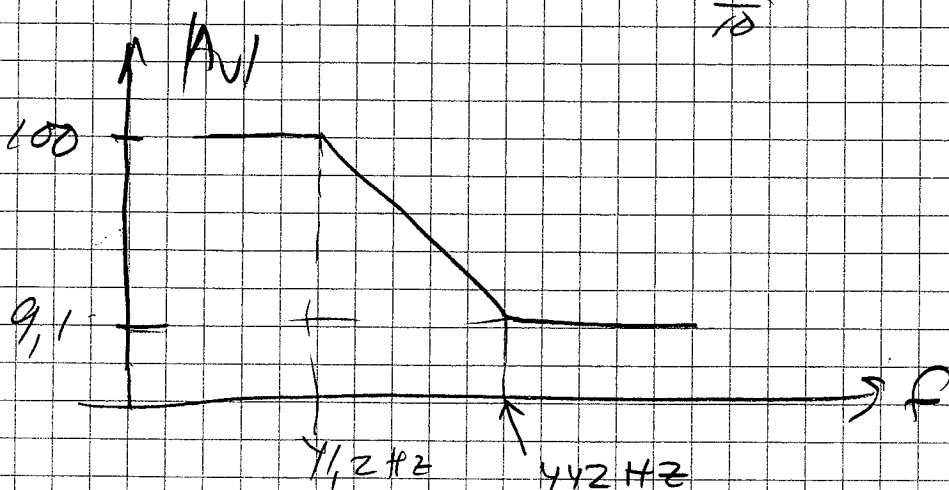
$$f \rightarrow 0 \Rightarrow A_u = - \frac{10R}{\frac{R}{10}} = \underline{-100}$$



B3/

Formelsammlung

$$\omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$Q = \frac{\sqrt{C_2 R_2}}{\sqrt{R_1} \cdot (C_1 + C_2)}$$

$$A_U = \frac{\omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$s^2 + s \frac{\omega_0}{Q} + \omega_0^2 = 0$$

$$s_{1,2} = -\frac{\omega_0}{2Q} \pm \sqrt{\left(\frac{\omega_0}{2Q}\right)^2 - \omega_0^2} =$$

$$= -\frac{\omega_0}{2Q} \pm j \sqrt{\omega_0^2 \left(1 - \left(\frac{1}{2Q}\right)^2\right)} = -\frac{\omega_0}{\sqrt{2}} \pm j \frac{\omega_0}{\sqrt{2}}$$

$$\omega_0 = 5 \cdot 10^4 \text{ rad/s}$$

$$\therefore \frac{\omega_0}{2Q} = \frac{\omega_0}{\sqrt{2}} \Rightarrow Q = \frac{1}{\sqrt{2}} \quad (2Q = \sqrt{2})$$

$$\cancel{\omega_0} \sqrt{1 - \left(\frac{1}{2Q}\right)^2} = \frac{\omega_0}{\sqrt{2}} \Rightarrow \sqrt{1 - \left(\frac{\sqrt{2}}{2 \cdot 1}\right)^2} = \frac{1}{\sqrt{2}} \quad \text{OK!}$$

$$\therefore (5 \cdot 10^4)^2 = \frac{1}{R_1 R_2 \cdot (15 \cdot 10^{-9})^2}$$

$$\Rightarrow 5,625 \cdot 10^7 = \frac{1}{R_1 R_2} \Rightarrow R_1 R_2 = 1,777 \cdot 10^6$$


$$\frac{1}{\sqrt{2}} = \frac{\sqrt{R_2} \cdot 8}{\sqrt{R_1} \cdot 24} \Rightarrow \frac{R_2}{R_1} = 2$$

$$\Rightarrow R_1 \cdot R_1 \cdot 2 = 1,777 \cdot 10^6 \Rightarrow R_1 = \underline{942 \Omega}$$


$$\Rightarrow R_2 = 2 R_1 = \underline{\underline{1886 \Omega}}$$

84/

$U_{out} = 12V$

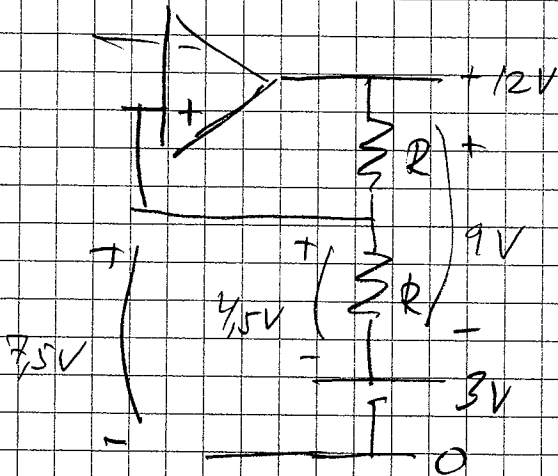


$U_{out} = -12V$

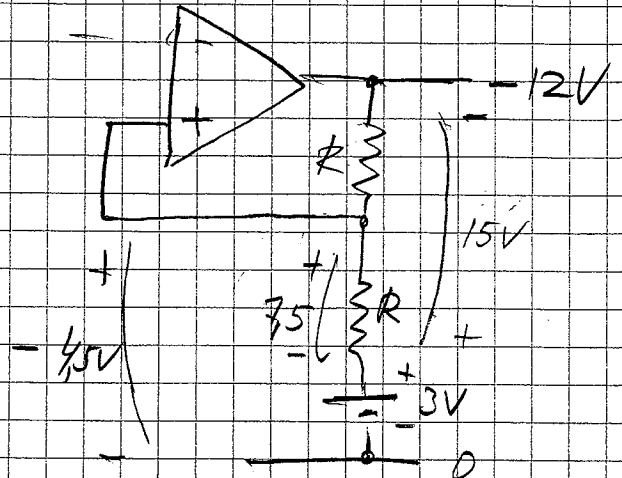

$\therefore$  Umschlag bei  $U_C = +7,5V$

Umschlag bei  $U_C = -7,5V$

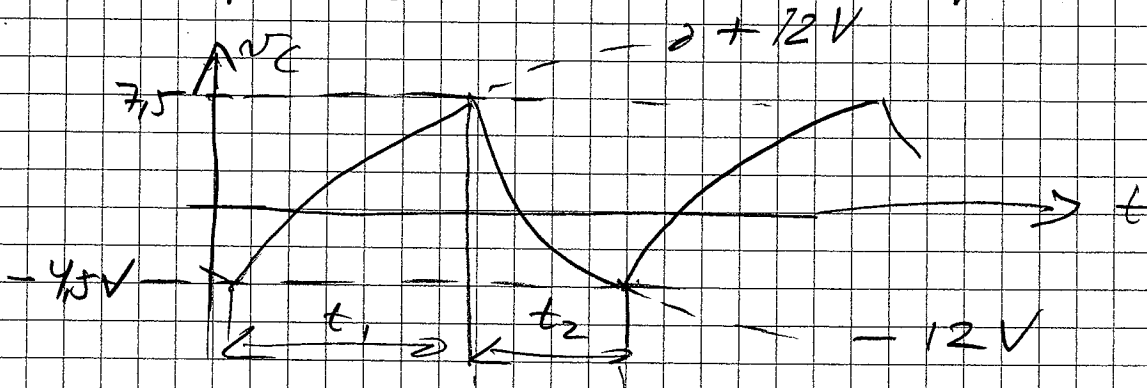


$$t_1 = \tau \ln \frac{A}{B} = R_f \cdot C \ln \frac{12 + 7,5}{12 - 7,5} = \frac{4 \cdot 10^3 \cdot 150 \cdot 10^{-9}}{600 \cdot 10^{-6}} \ln \frac{19,5}{4,5}$$

$$= 7,7956 \cdot 10^{-4} \text{ s}$$

$$t_2 = R_f \cdot C \ln \frac{12 + 7,5}{12 - 7,5} = 6 \cdot 10^{-4} \ln \frac{19,5}{7,5} = 5,733 \cdot 10^{-4} \text{ s}$$

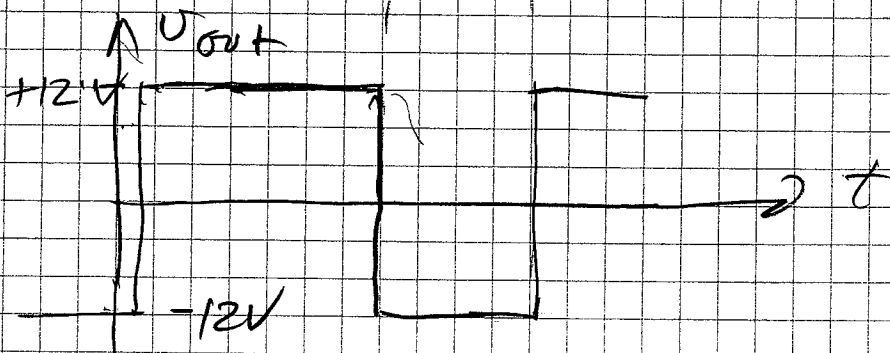
$$f = \frac{1}{t_1 + t_2} = \underline{\underline{739 \text{ Hz}}}$$



B3/  
a)

$$P_{\text{Diss, max}} = \frac{150^\circ - 40^\circ \text{C}}{4,4^\circ \text{C/W}} = 25 \text{ W} \text{ för en transistor.}$$

b)

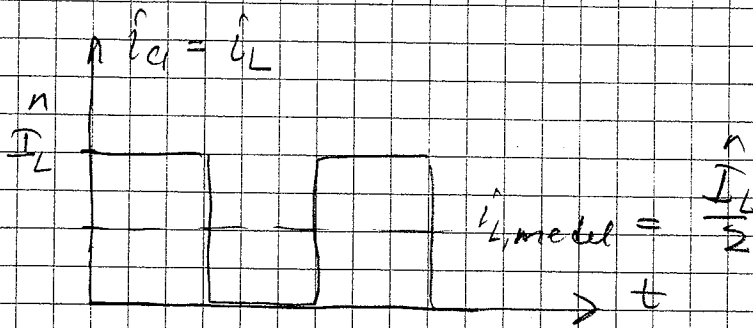

För båda matningsspänningarna  $V_{CC}$

$$P_{\text{Batt}} = 2 \cdot V_{CC} \cdot \frac{\hat{I}_L}{2} \text{ och båda transistorerna}$$

$$P_{\text{Diss}} = P_{\text{Batt}} - P_E - P_L = V_{CC} \cdot \hat{I}_L - \frac{\hat{I}_L^2}{2} (R_E + R_L)$$

Sök:  $P_{\text{Diss, max}}$

$$\frac{dP_{\text{Diss}}}{d\hat{I}_L} = V_{CC} - \hat{I}_L (R_E + R_L) = 0$$

$$\Rightarrow \hat{I}_L = \frac{V_{CC}}{2(R_E + R_L)}$$

$$\begin{aligned} \therefore 2 \cdot 25 \text{ W} &= V_{CC} \frac{V_{CC}}{2(R_E + R_L)} - \frac{V_{CC}^2 \cdot (R_E + R_L)}{4(R_E + R_L)^2} \\ &= \frac{V_{CC}^2}{4(R_E + R_L)} = \frac{30^2}{4(R_E + R_L)} \Rightarrow R_E + R_L = 4,5 \Omega \end{aligned}$$

$$\Rightarrow R_L = 4,5 - 0,4 = 4,1 \Omega$$

$$\hat{I}_{L, \text{max}} = \frac{(30 - 4) \text{ V}}{4,5 \Omega} = 5,78 \text{ A}$$

$$P_{\text{ut, max}} = \hat{I}_L^2 \cdot R_L = 5,78^2 \cdot 4,1 = \underline{\underline{137 \text{ W}}}$$