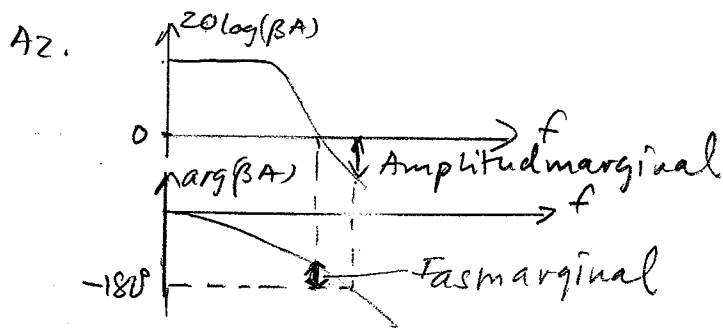


Svar till tenta Elektronik forts. 14/1-04

A1. -60dB/decad



A3. Max  $I_Z$  då  $I_{R_L}$  är min. ( $\frac{10}{100} = 0,1A$ ) och  $V_{IN}$  är max

$$\frac{V_{IN,max} - 10V}{R} = I_{R_L,min} + I_{Z,max}$$

$$I_{Z,max} = \frac{P_{Z,max}}{10V} = \frac{2}{10} = 0,2A$$

$$\Rightarrow \frac{V_{IN,max} - 10V}{50\Omega} = \frac{10V}{50\Omega} + 0,1A + 0,2A = 0,5A$$

$$\Rightarrow V_{IN,max} = 50 \cdot 0,5 = \underline{25V}$$

$I_Z = 0$  då  $V_{IN,min}$  och  $I_{R_L,max}$

$$\frac{V_{IN,min} - 10V}{50\Omega} = \frac{10}{50} \Rightarrow V_{IN,min} = \underline{20V}$$

A4. Spän. delning på utgångar

$$V_{ZK} = V_{out} \frac{R_2}{R_1 + R_2} \Rightarrow V_{out} = \underline{18V}$$

A5.

$$I_{C5} = \frac{2V_{CC} - 2V_{BE}}{R} = \frac{2 \cdot 11,3V}{15k\Omega} \approx 1,5mA \approx I_{C4}$$

$$I_{C2} = I_{C3} \approx \frac{I_{C4}}{2} = \underline{0,75mA}$$

A6.


$$f_{out} = n \cdot f_{in}$$

A7.

$$f_L = \frac{1}{2\pi R_1 C} \approx \underline{7,2Hz}$$

A8. a) c) och f)

A9.

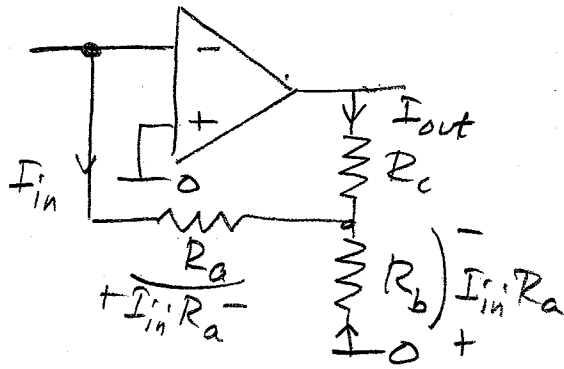

Kirch. Stromlag

$$I_{in} + I_{out} + \frac{I_{in}' R_a}{R_b} = 0$$

$$\Rightarrow \frac{I_{out}}{I_{in}} = - \left( 1 + \frac{R_a}{R_b} \right)$$

A10.


$$\left( \frac{V_{ref}}{2R} + \frac{V_{ref}}{16R} \right) \cdot 4R = -V_{out}$$

$$\Rightarrow V_{ref} \left( 2 + \frac{1}{4} \right) = 5 \cdot 2,25 = +11,25V = -V_{out}$$

$$\therefore V_{out} = -11,25V$$

B1.

Ekv. signalschema

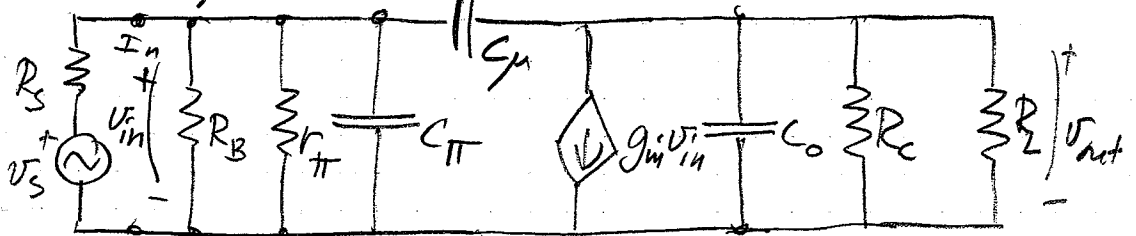

$$f_T = \frac{\beta}{2\pi r_{\pi} (C_{\pi} + C_{\mu})} \Rightarrow C_{\pi} + C_{\mu} = \frac{\beta}{f_T \cdot 2\pi r_{\pi}}$$

$$= \frac{200}{200 \cdot 10^6 \cdot 2\pi \cdot 2,3 \cdot 10^3} = 69,2 \text{ pF} \Rightarrow C_{\pi} = 66,2 \text{ pF}$$

$$C_{in, \text{Miller}} = C_{\mu} (1 - A_v)$$

$$A_v = -g_m \cdot R_L' = -\frac{\beta}{r_{\pi}} \cdot (R_c \parallel R_L) = -208,799$$


$$\Rightarrow C_{in, \text{Miller}} = 3 \text{ pF} (1 + 208,7) = 629,1 \text{ pF}$$

$$C_{in} = C_{in, \text{Miller}} + C_{\pi} = 629,1 + 66,2 = 695,3 \text{ pF}$$

$$C_{out} = C_o + C_{out, \text{Miller}} = C_o + C_{\mu} \frac{A_v - 1}{A_v} =$$

$$= 5 + 3 \frac{-208,7}{-208,7} \approx 8 \text{ pF}$$

Förenklat ekv. signalschema

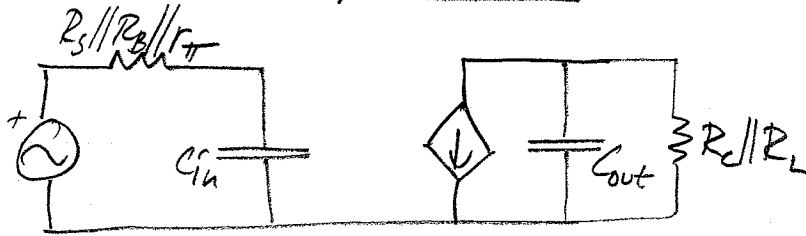

$$f_{H, in} = \frac{1}{2\pi (R_s || R_B || r_T) \cdot C_{in}} = \frac{1}{2\pi \cdot 1,57 \cdot 10^3 \cdot 695,3 \cdot 10^{-11}}$$

$$= \underline{146 \text{ kHz}}$$

$$f_{H, out} = \frac{1}{2\pi \cdot 2,4 \cdot 10^3 \cdot 8 \cdot 10^{-12}} = \underline{8,3 \text{ MHz}}$$

$$f_{H, tot} = \frac{1}{\frac{1}{f_{H, in}} + \frac{1}{f_{H, out}}} \approx \underline{143 \text{ kHz}}$$

82.

$$A_V = \frac{R_2 || (R_3 + \frac{1}{sC}) + R_1}{R_1} = \frac{R_2 (R_3 + \frac{1}{sC})}{R_1 + R_3 + \frac{1}{sC}} + R_1 =$$

$$= \frac{R_2 (R_3 + \frac{1}{sC}) + R_1 (R_2 + R_3 + \frac{1}{sC})}{R_1 (R_2 + R_3 + \frac{1}{sC})} =$$

$$= \frac{R_2 R_3 + R_2 \frac{1}{sC} + R_1 R_2 + R_1 R_3 + R_1 \frac{1}{sC}}{R_1 R_2 + R_1 R_3 + R_1 \frac{1}{sC}} \cdot \frac{sC}{sC} =$$

$$= \frac{(R_2 R_3 + R_1 R_2 + R_1 R_3) \cdot sC + (R_1 + R_2)}{(R_1 R_2 + R_1 R_3) \cdot sC + R_1}$$

Nollställe:  $(R_2 R_3 + R_1 R_2 + R_1 R_3) \cdot sC + R_1 + R_2 = 0$

$$\Rightarrow s = - \frac{R_1 + R_2}{(R_2 R_3 + R_1 R_2 + R_1 R_3) C} \Rightarrow \omega_n = 2453 \text{ rad/s}$$

$$\Rightarrow f_n = \underline{390 \text{ Hz}}$$

Pol:  $(R_1 R_2 + R_1 R_3) \cdot sC + R_1 = 0$


$$\Rightarrow s = - \frac{R_1}{(R_1 R_2 + R_1 R_3) C} \Rightarrow \omega_n = 272 \text{ rad/s}$$

$$\Rightarrow f_p = \underline{43 \text{ Hz}}$$


forts.  
B2/

$$A_v = \frac{R_2 // (R_3 + R_1)}{R_1} = 11,2 \text{ ggr da } f \rightarrow \infty \text{ (Kondensatorn \u00e4r kortslutning)}$$
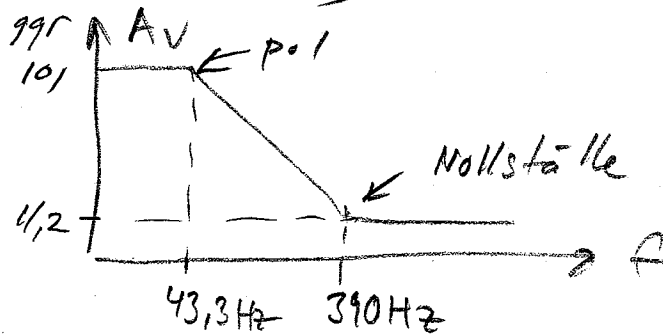
$$A_v = \frac{R_2 + R_1}{R_1} = 101 \text{ ggr da } f \rightarrow 0 \text{ (Kondensatorn \u00e4r avbr\u00f6tt)}$$



B3/

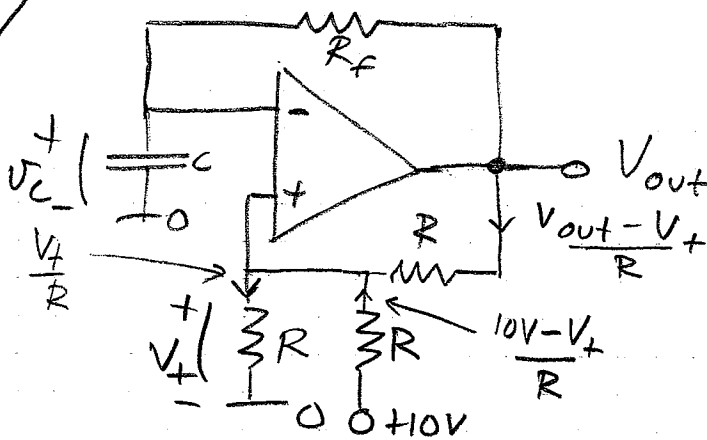

Kirch. str\u00f6mlag


$$\frac{V_{out} - V_+}{R} + \frac{10V - V_+}{R} = \frac{V_+}{R}$$

$$\Rightarrow V_+ = \frac{V_{out} + 10V}{3}$$

Omslag da  $v_c = V_+ = \frac{V_{out} + 10V}{3}$

$$\Rightarrow V_{out} = 10V \Rightarrow V_+ = \frac{20}{3} = 6,67V$$
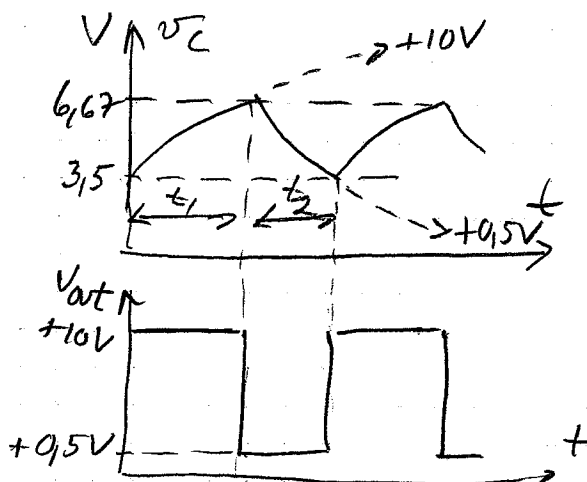
$$\Rightarrow V_{out} = 0,5V \Rightarrow V_+ = \frac{10,5}{3} = 3,5V$$



$$\Delta t = T \ln \frac{A}{B} \text{ ger}$$

$$t_1 = R_f C \ln \frac{10 - 3,5}{10 - 6,67} = 20 \mu s$$

$$t_2 = R_f C \ln \frac{6,67 - 0,5}{3,5 - 0,5} = 21,6 \mu s$$

$$f = \frac{1}{t_1 + t_2} = 24 \text{ kHz}$$

B4/ Total termisk resistans  $\theta_{tot} = 1,5 + 3 + 0,5 = 5 \text{ } ^\circ\text{C/W}$

$$\text{Kollektorförlusten } P_{D, \max} = \frac{T_J - T_A}{\theta_{tot}} = \frac{175 - 35}{5} = \underline{28 \text{ W}} \text{ (en transistor)}$$

För båda transistorerna gäller:

$$P_D = \frac{2 \cdot V_{CC} \cdot V_m}{\pi(R_L + R_E)} - \frac{V_m^2}{2(R_L + R_E)} \quad (= P_{\text{Batt}} - P_{\text{Last}})$$

Derivering för att få  $P_{D, \max}$

$$\frac{dP_D}{dV_m} = \frac{2 \cdot V_{CC}}{\pi(R_L + R_E)} - \frac{2 \cdot V_m}{2(R_L + R_E)} = 0$$

$$\Rightarrow V_m = \frac{V_{CC} \cdot 2}{\pi}$$


$$\therefore P_{D, \max} = \frac{2 \cdot V_{CC} \cdot V_{CC} \cdot 2}{\pi(R_L + R_E)\pi} - \frac{\left(\frac{V_{CC} \cdot 2}{\pi}\right)^2}{2(R_L + R_E)} = \frac{V_{CC}^2 \cdot 2}{\pi^2(R_L + R_E)}$$

$$\therefore 2 \cdot 28 \text{ W} = \frac{30^2 \cdot 2}{\pi^2(R_L + R_E)} \Rightarrow R_L + R_E = 3,26 \Omega$$

$$\Rightarrow R_L = 2,76 - 0,5 = \underline{2,76 \Omega}$$

$$I_{\text{out}, \max} = \frac{30 - 3}{R_E + R_L} = \frac{27}{3,26} = 8,28 \text{ A}$$

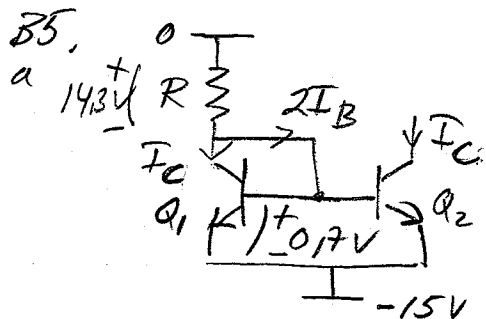
$$P_{\text{out}, \max} = \frac{1}{2} \cdot I_{\text{out}, \max}^2 \cdot R_L = \frac{8,28^2 \cdot 2,76}{2} \approx \underline{95 \text{ W}}$$



$$(I_C + 2I_B) \cdot R = 14,3 \text{ V}$$

$$\Rightarrow (I_C + 2 \frac{I_C}{\beta}) \cdot 3,3 \text{ k}\Omega = 14,3 \text{ V}$$

$$\Rightarrow I_C = 4,25 \text{ mA}$$

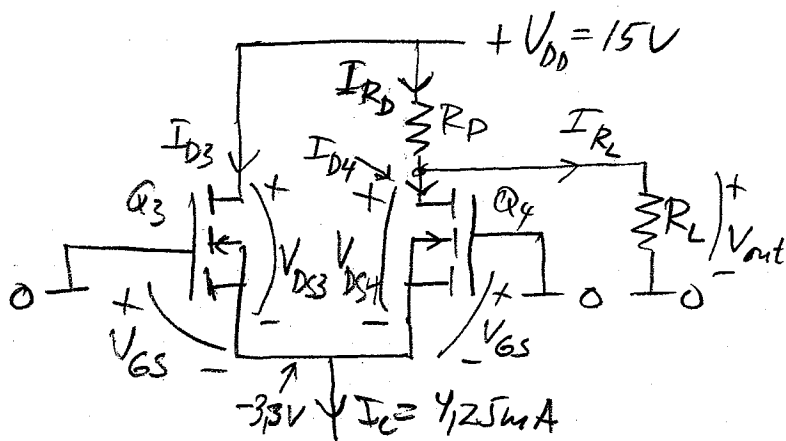

$$I_{D3} = I_{D4} = \frac{4,25}{2} = 2,125 \text{ mA}$$

$$I_{D3} = I_{D4} = K \cdot (V_{GS} - V_{to})^2 = \frac{1}{2} k_p \frac{W}{L} (V_{GS} - V_{to})^2 = 1,25 \text{ mA/V}^2 (V_{GS} - 2)^2 = 2,125 \text{ mA}$$

$$\Rightarrow V_{GS} = 3,3 \text{ V}$$

$$V_{DS3} = 15 + 3,3 = 18,3 \text{ V}$$

$$18,3 \text{ V} = I_{R_D} \cdot R_D + V_{DS4}$$

Kirch. ström lawe

$$I_{R_D} = I_{R_L} + I_{D4} = I_{R_L} + 2,125 \text{ mA}$$

$$\text{där } I_{R_L} = \frac{3,3 \text{ V} + V_{DS4}}{R_L} = \frac{3,3}{10} \text{ mA} + \frac{V_{DS4}}{10 \text{ k}\Omega}$$

$$\Rightarrow 18,3 \text{ V} = (0,33 \text{ mA} + \frac{V_{DS4}}{10 \text{ k}\Omega}) \cdot 6,8 \text{ k}\Omega + V_{DS4}$$

$$\Rightarrow V_{DS4} = 3,63 \text{ V}$$

$$b) A_{vds} = -\frac{1}{2} g_m \cdot (r_d \parallel R_D \parallel R_L) \text{ där } g_m = 2 \sqrt{k \cdot I_{D4}} = 2 \cdot \sqrt{1,25 \cdot 2,12} = 3,26 \text{ mA/V}$$

$$\Rightarrow A_{vds} = -\frac{1}{2} \cdot 3,26 \cdot (50 \parallel 6,8 \parallel 10) = -6,199 \text{ V}$$

$$c) CMRR_S = \frac{1}{2} + g_m R_{SB} = \frac{1}{2} + g_m r_O = \frac{1}{2} + 3,26 \cdot 150 = 490,99 \text{ V}$$